





Effect of R_L load resistor in red

$$L \frac{di_L}{dt} + V_C(t) = V_I$$

$$i_L = -\frac{1}{L} V_C + \frac{V_I}{L}$$

$$i_L = C \frac{dV_C}{dt} = C \dot{V}_C + \frac{V_C}{R_L}$$

$$\dot{V}_C = \frac{1}{C} i_L - \frac{V_C}{R_L C}$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{V}_C \end{bmatrix} = \underbrace{\begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R_L C} \end{bmatrix}}_{\underline{A}} \underbrace{\begin{bmatrix} i_L \\ V_C \end{bmatrix}}_{\underline{x}} + \underbrace{\begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix}}_{\underline{B}} V_I$$

when s_1 closed, (d(t) of the time)

$$\begin{bmatrix} \dot{i}_L \\ \dot{V}_C \end{bmatrix} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & -\frac{1}{R_L C} \end{bmatrix} \begin{bmatrix} i_L \\ V_C \end{bmatrix} + 0$$

when s_2 is closed ((1-d(t)) of the time)

Averaging:

$$\dot{\underline{x}} = \underline{A} \underline{x} + \underline{B} \cdot d(t) V_I(t)$$

Perturbation Method:

$$d_p(t) = D_D + d_d(t) \quad \& \quad V_I(t) = V_I + v_i(t)$$

$$d_p(t) V_I(t) = (D_D + d_d(t)) (V_I + v_i(t))$$

$$\approx D_0 V_I + V_I d_d(t) + D_0 v_i(t) + \cancel{d_d(t) V_i(t)} \xrightarrow{\approx 0}$$

$$x_s(t) = \underline{x}_s + \underline{x}_s(t)$$

$$\dot{\underline{x}}_s(t) = \cancel{\frac{d\underline{x}_s}{dt}} + \dot{\underline{x}}_s(t)$$

$$\dot{\underline{x}}_s(t) = \underline{A} (\underline{x}_s + \underline{x}_s(t)) + \underline{B} (D_0 V_I + V_I d_d(t) + D_0 v_i(t))$$

$$\dot{\underline{x}}_s(t) = \underline{A} \underline{x}_s + \underline{B} D_0 V_I + \underline{A} \underline{x}_s(t) + \underline{B} [V_I, D_0] \begin{bmatrix} d_d(t) \\ v_i(t) \end{bmatrix}$$

setting small signals to zero:

$$\underline{A} \underline{x}_s + \underline{B} D_0 V_I = 0$$

$$\underline{x}_s = -\underline{A}^{-1} \underline{B} D_0 V_I \quad \text{This is the Q point}$$

$$\dot{\underline{x}}_s(t) = \underline{A} \underline{x}_s(t) + \underbrace{\begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} [V_I \ D_0]}_{\begin{bmatrix} V_I/L & D_0 \\ 0 & 0 \end{bmatrix}} \begin{bmatrix} d_d(t) \\ v_i(t) \end{bmatrix}$$

This last is the small signal model.

Let's find the Q point:

$$\underline{A}^{-1} = \begin{bmatrix} 0 & -\frac{1}{L} \\ \frac{1}{C} & \frac{R}{L} \end{bmatrix}^{-1} = LC \begin{bmatrix} \frac{1}{RL} & \frac{1}{L} \\ -\frac{1}{C} & 0 \end{bmatrix} = \begin{bmatrix} \frac{1}{RL} & C \\ -L & 0 \end{bmatrix}$$

$$\begin{bmatrix} \bar{I}_L \\ V_C \end{bmatrix} = \underline{x}_s = -\underline{A}^{-1} \underline{B} D_0 V_I = \begin{bmatrix} \frac{L}{RL} & -C \\ L & 0 \end{bmatrix} \begin{bmatrix} \frac{1}{L} \\ 0 \end{bmatrix} D_0 V_I = \begin{bmatrix} \frac{D_0 V_I}{RL} \\ D_0 V_I \end{bmatrix}$$