
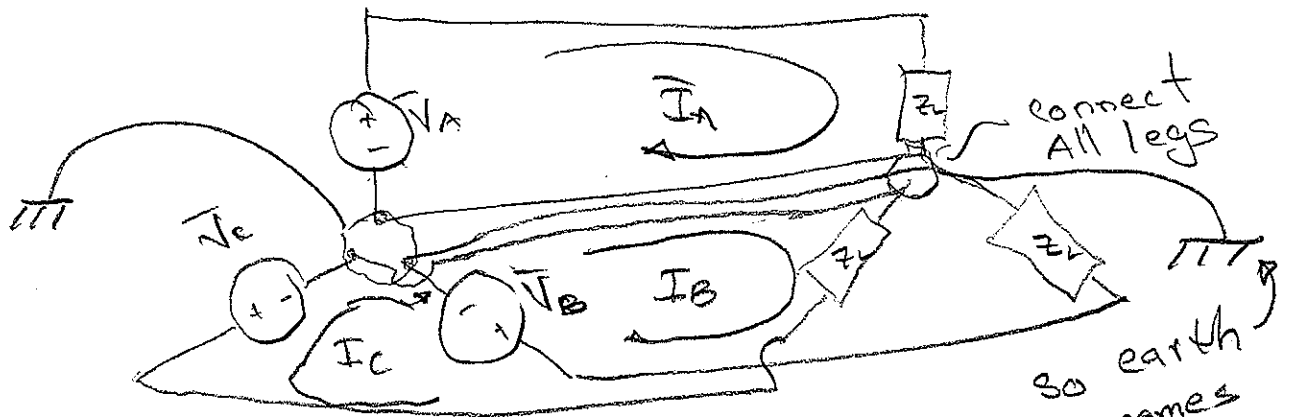
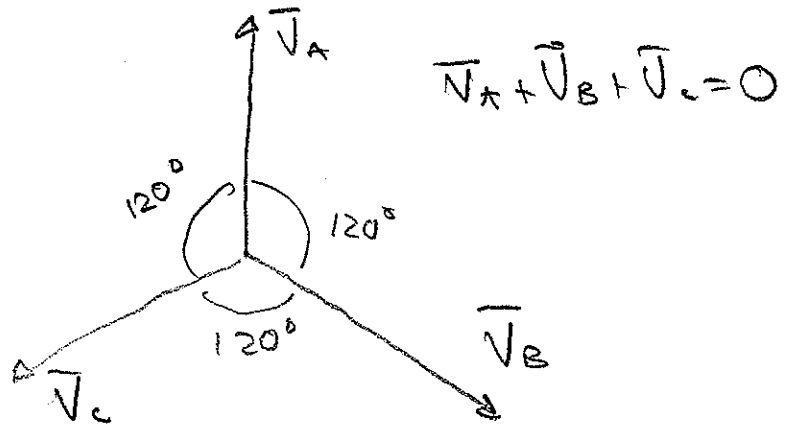
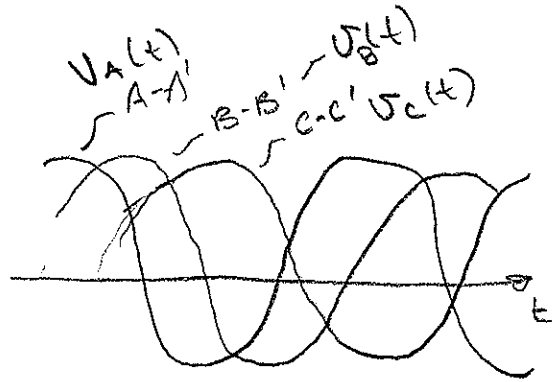




Three Phase

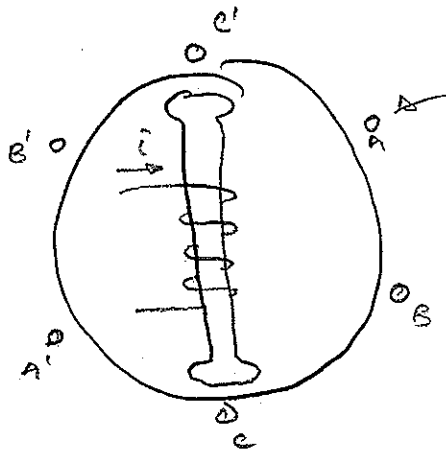

so earth becomes the return leg.

$$\vec{I}_A = \frac{\vec{V}_A}{Z_L} ; \vec{I}_B = \frac{\vec{V}_B}{Z_L} ; \vec{I}_C = \frac{\vec{V}_C}{Z_L}$$

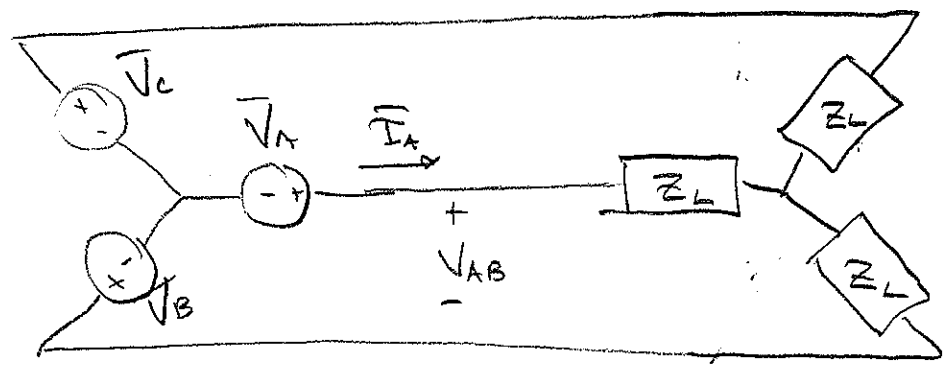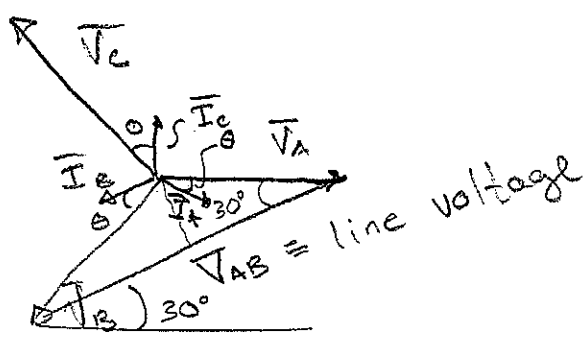Note:  $\vec{I}_A + \vec{I}_B + \vec{I}_C = 0$  if  $Z_L$ 's are all the same so the return leg isn't actually needed if it is balanced. Balanced Y-Y connection.



$$|\vec{V}_{AB}| = 2 \cos 30^\circ |\vec{V}_A| = \sqrt{3} |\vec{V}_A|$$

$$\vec{V}_{AB} = \vec{V}_A e^{j30^\circ}$$

For Y-Y the line currents equal the phase currents.

$$P_A = |\vec{V}_A| |\vec{I}_A| \cos \theta$$

$$P = P_A (3) = 3 \vec{V}_A \vec{I}_A \cos \theta = 3 \frac{|\vec{V}_{AB}|}{\sqrt{3}} |\vec{I}_A| \cos \theta$$


$$= \sqrt{3} |\vec{V}_{AB}| |\vec{I}_{AB}| \cos \theta$$

$$Q = \sqrt{3} |\vec{V}_{AB}| |\vec{I}_{AB}| \sin \theta$$

$$S = P + jQ = \sqrt{3} |\vec{V}_{AB}| |\vec{I}_A| e^{j\theta}$$

Note: This didn't go boom!

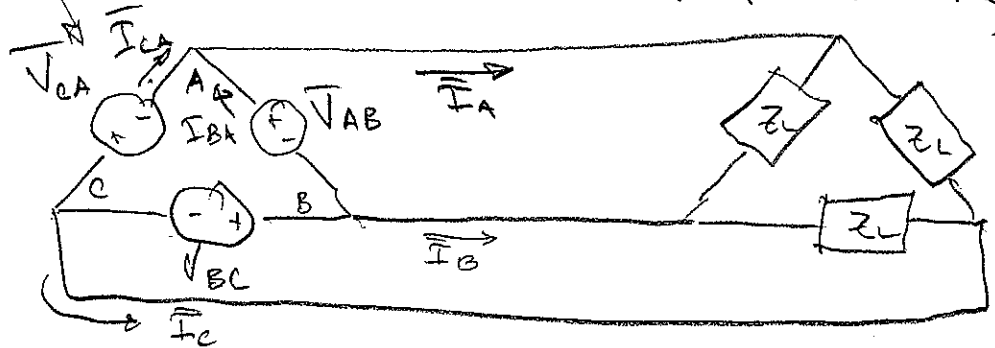
The  $\Delta-\Delta$  is a dual of the Y-Y.



$$\vec{V}_{CA} + \vec{V}_{BC} + \vec{V}_{AB} = 0$$



Now the line to line voltages are the same as the phase voltages. The line currents are given by:
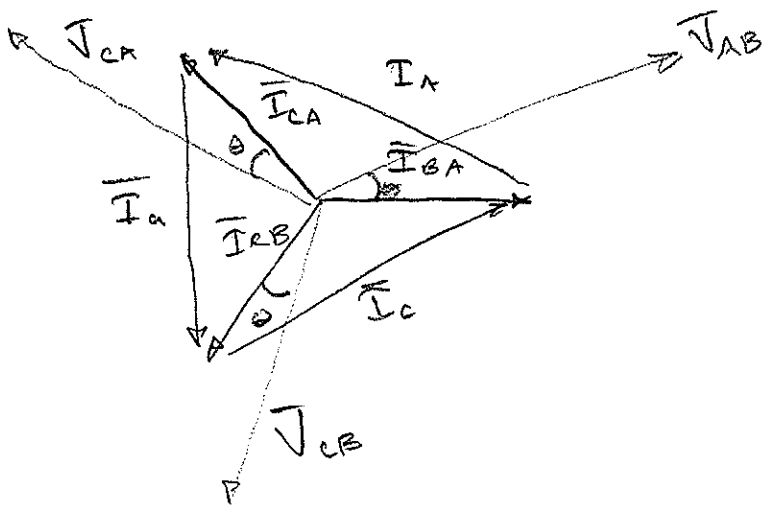
$$\bar{I}_A = \bar{I}_{CA} + \bar{I}_{BA} = \sqrt{3} \bar{I}_{CA} e^{j30^\circ}$$



$$S = \sqrt{3} V_L I_L e^{j\theta}$$

for either Y-Y or Δ-Δ.

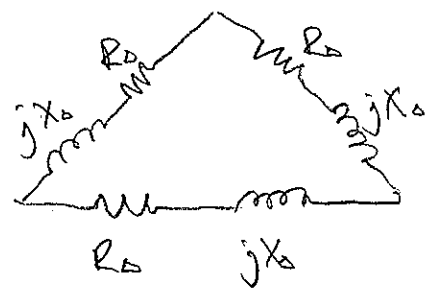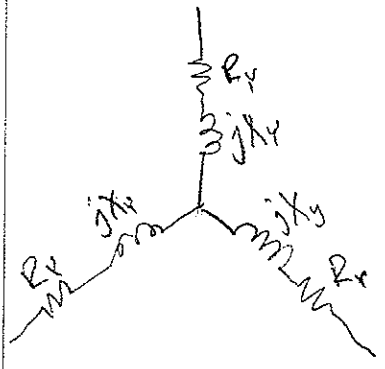

If the power is the same,  $P = \sqrt{3} V_L I_L \cos \theta$ , and they are connected to the same generator, then  $V_L, I_L$  are the same. Assume  $\theta$  is the same.

$$Z_Y = \frac{V_{\phi Y}}{I_{\phi Y}} = \frac{V_L}{\sqrt{3} I_L} \qquad Z_{\Delta} = \frac{V_{\phi \Delta}}{I_{\phi \Delta}} = \frac{V_L \sqrt{3}}{I_L}$$


$$\frac{Z_Y}{Z_{\Delta}} = \frac{1}{3}$$

If we want  $Z_{eq}$  to be the same, then  $\theta$  is the same.

Rod did P 1-27 as an example

How to Measure Power in 3-Phase  
using two Wattmeters

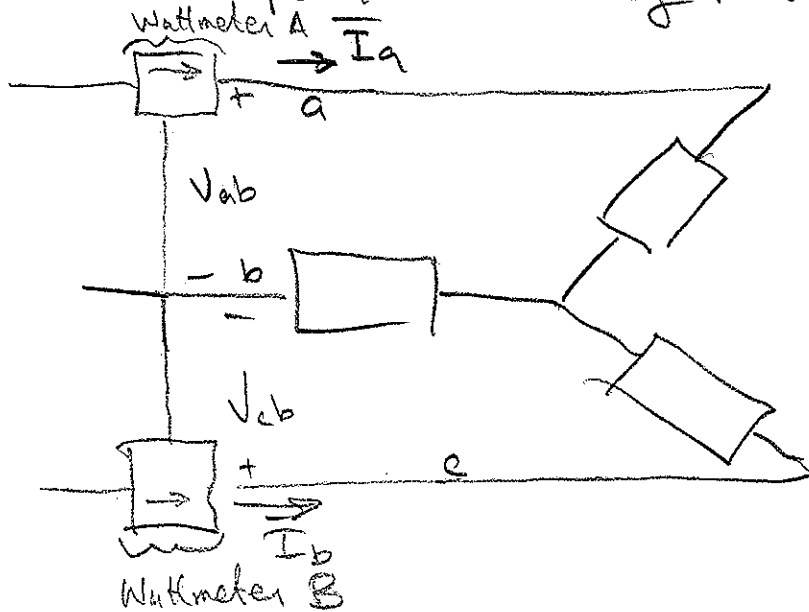The neutral point is usually not available




Think of b as the "ground" leg.

$$P_{total} = P_A + P_B$$

$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t} + \nabla \times (\vec{v} \times \vec{B})$$
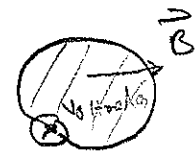
$$\oint \vec{E} \cdot d\vec{l} = -\frac{\partial}{\partial t} \int \vec{B} \cdot d\vec{S} + \oint (\vec{v} \times \vec{B}) \cdot d\vec{l}$$




Faraday's Law


$$\nabla \cdot \vec{D} = \rho$$

$$\oint \vec{D} \cdot d\vec{S} = \int \rho dv \quad \left. \vphantom{\int \rho dv} \right\} \text{ Gauss}$$

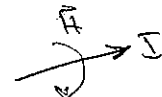
$$\nabla \cdot \vec{B} = 0 \quad \text{or} \quad \oint \vec{B} \cdot d\vec{S} = 0$$


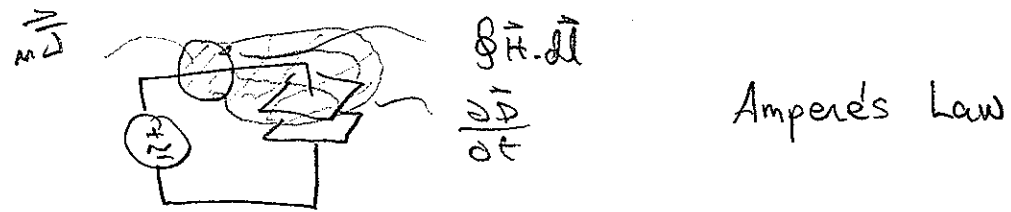
$$\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t} \quad \text{or} \quad \oint \vec{H} \cdot d\vec{l} = \int (\vec{J} + \frac{\partial \vec{D}}{\partial t}) \cdot d\vec{S}$$



Review of Electromagnetics

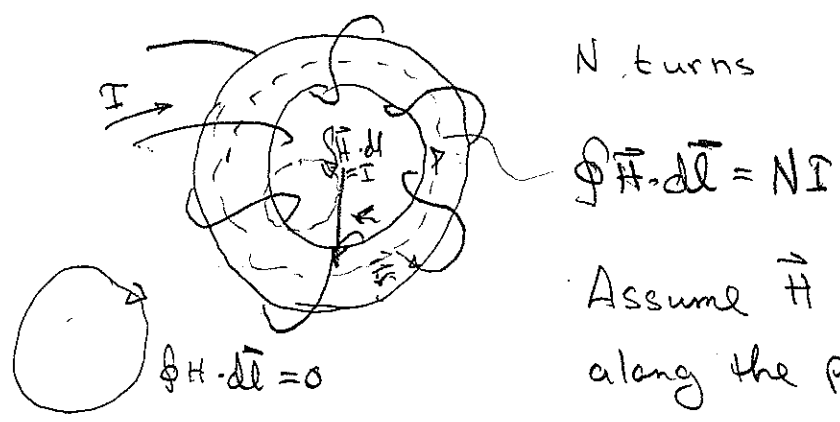

Assume  $\vec{H}$  is constant along the path.

$$H(2\pi r) = NI \Rightarrow \vec{H} = \frac{NI}{2\pi R} \hat{a}_\phi = \frac{NI}{l} \hat{a}_\phi$$


$H$  (Ampere turns / meter)       $\vec{B} = \mu \vec{H}$  (Webers / square meter) = (tesla)

or (Gause) or (lines)

Now find the flux going through the core. Assume  $|\vec{B}|$  is constant over the cross section.


$$\Phi = \int \vec{B} \cdot d\vec{s} = B \pi r^2 = \frac{\mu NI}{l} A = \frac{NI}{\frac{l}{\mu A}} = \Phi$$
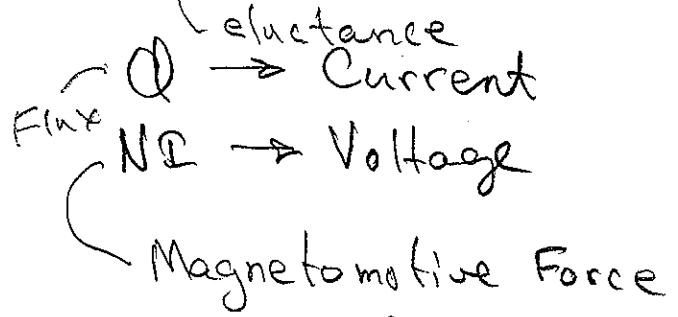
$$R = \frac{l}{\mu A} \text{ like } R = \frac{l}{\sigma A}$$



$$\Phi = \frac{mmf}{R} = \frac{\mathcal{F}}{R}$$

Like Ohm's Law

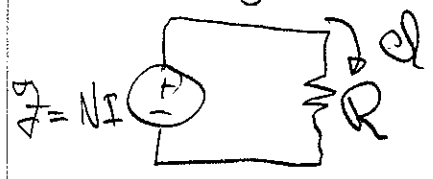

$$\nabla \cdot \vec{B} = 0 \Rightarrow \text{KCL equivalent}$$

$$v = L \frac{di}{dt} = N \frac{d\phi}{dt}$$

$$Li = N\phi \quad \Rightarrow \quad L = \frac{N\phi}{i}$$

Rod has the styrofoam toroid setup.

$$i = 1 \text{ A}$$

$$N = 410$$

$$R = 10.5 \text{ cm}$$

$$r = 2 \text{ cm}$$

$$\mathcal{F} = NI = 410$$

$$H = \frac{NI}{2\pi R} = 621.5 \frac{\text{Amperturns}}{\text{meter}}$$


$$B = \mu_0 H = 4\pi \times 10^{-7} (621.5) = 7.8 \times 10^{-4} \text{ T}$$

$$= 7.8 \text{ Gauss}$$




Using the Gauss meter we measure, 7.5 Gauss.

$$L = \frac{N\phi}{I} = \frac{410 (7.8 \times 10^{-4}) \pi (0.02)^2}{1} = 402 \text{ mH}$$

Wavetek measures  $L = 38 \text{ mH}$ .

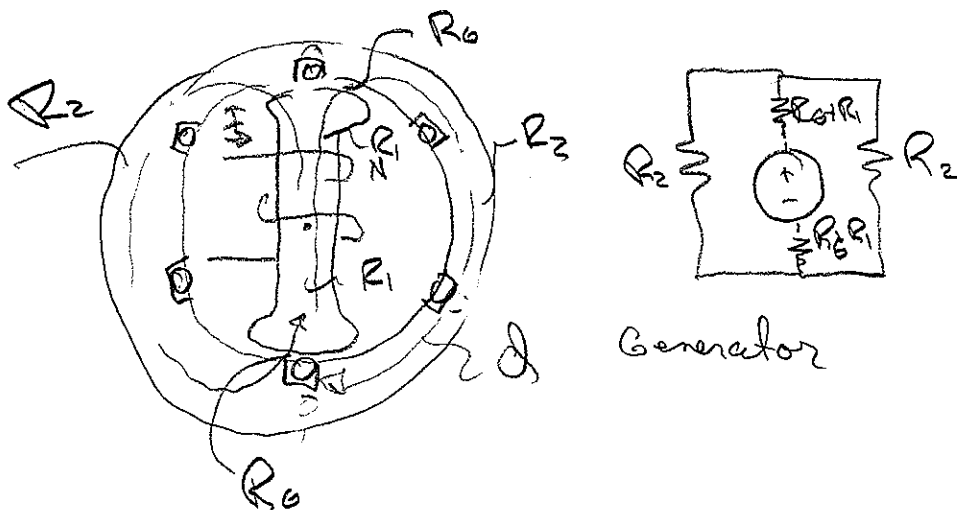

Rod showed how to magnetize a paperclip.

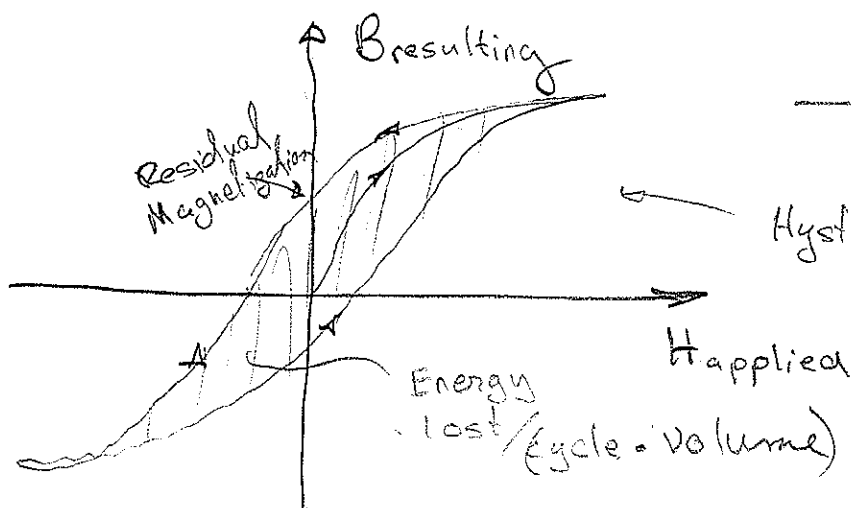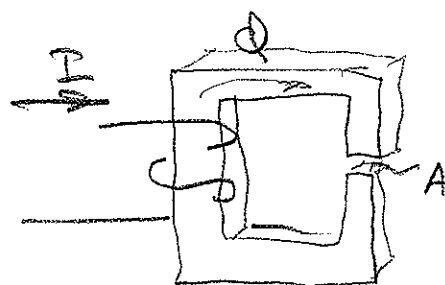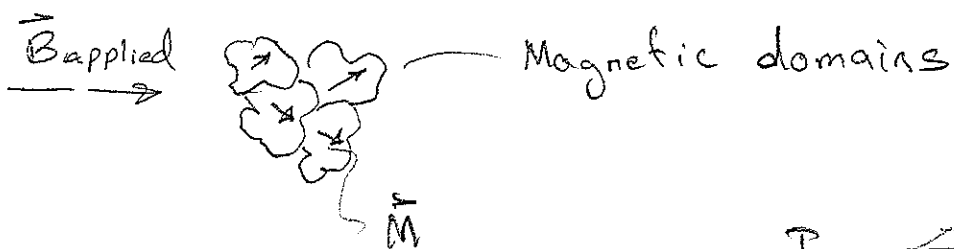

Hysteresis curve

$$\oint \vec{H} \cdot d\vec{l} = NI \Rightarrow H = \frac{NI}{l} \quad \Phi = \int \vec{B} \cdot d\vec{s} = BA$$

↑  
Applied


$\vec{B} \neq \mu \vec{H}$  because it is not linear

$$\frac{1}{2} \int \vec{B} \cdot \vec{H} \, dv \equiv E$$

$$\frac{1}{2} L i^2 = \frac{1}{2} \left( \frac{N\Phi}{i} \right) i^2 = \frac{1}{2} Ni\Phi = \frac{1}{2} HlBA$$

$$= \frac{1}{2} BH (\text{volume})$$
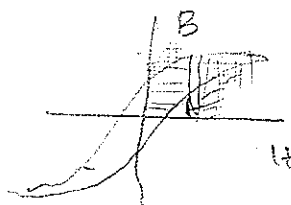
$$d\left(\frac{1}{2} BH\right) = \frac{1}{2} B dH + \frac{1}{2} H dB$$



This covers core losses.

22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



# Eddy Current Losses

Faraday's Law  $\Rightarrow$  voltages created in the iron core  $\Rightarrow$  creates eddy currents.



$$\oint \vec{E} \cdot d\vec{l} = -\frac{\partial \phi}{\partial t} + \oint (\vec{v} \times \vec{B}) \cdot d\vec{l}$$

Transformers use laminated cores.

No eddy currents in D.C.


$$+ \frac{H_c l_c}{R_c} -$$

Lab Experiment

$$Q_c = \frac{l_c}{\mu_0 A_c}$$

$$Q_g = \frac{l_g}{\mu_0 A_g}$$

Not a constant

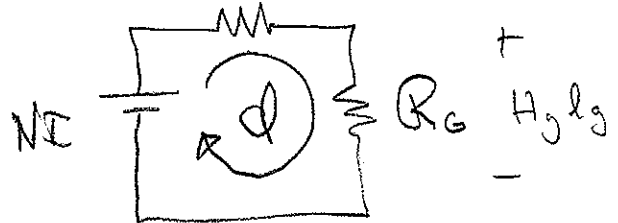

Not a good way to deal with this since core is non linear.

$$\text{So } \oint \vec{H} \cdot d\vec{l} = NI$$

$$H_g l_g + H_c l_c = NI$$

$$\underbrace{\phi R_g}_{B_g = \mu_0 H_g} = H_g l_g$$



Measure  $B_g$  & make B-H curve.

Include fringing  $A_g = (A_c + g)^2$

Now Rod does a load line analysis to do a graphical solution. Get his notes.



# Transformers

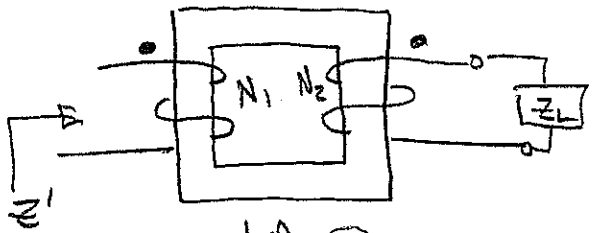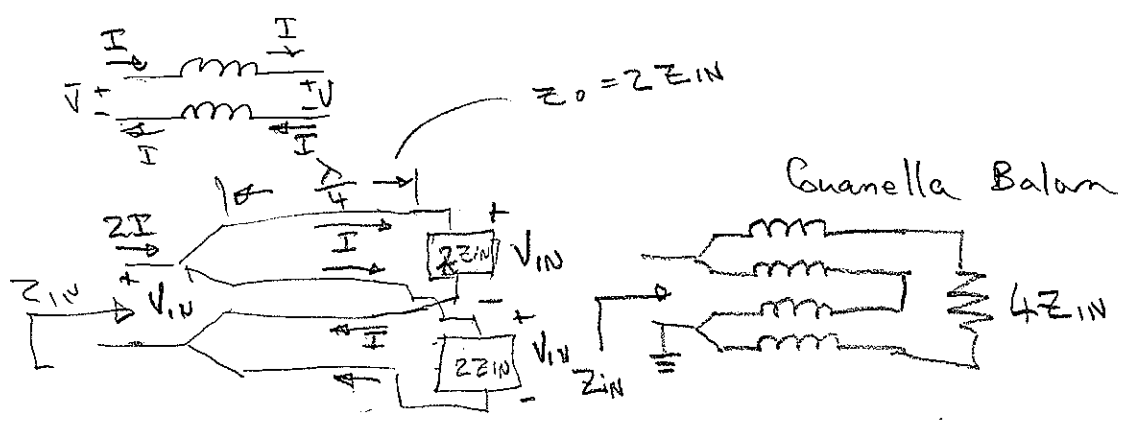


$$\begin{aligned}
 v_1 &= N_1 \frac{d\phi}{dt} \\
 v_2 &= N_2 \frac{d\phi}{dt}
 \end{aligned}
 \left. \vphantom{\begin{aligned} v_1 \\ v_2 \end{aligned}} \right\} \frac{v_1}{v_2} = \frac{N_1}{N_2} \equiv a$$

$$N_1 I_1 - N_2 I_2 = \oint \vec{H} \cdot d\vec{l} = 0$$

$$\frac{I_1}{I_2} = \frac{1}{a}$$
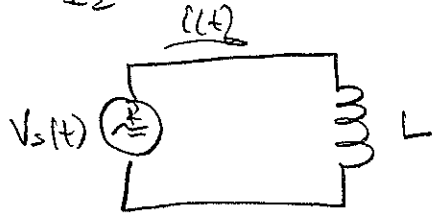
$$\frac{V_2}{I_2} = Z_L = \frac{1}{a^2} Z'$$



$$v = L \frac{di}{dt}$$

$$\phi = Li$$

$$i = \frac{N\phi}{L} = \frac{AS}{L} \frac{V_m}{2\pi f N} \sin(\omega t)$$

$$i = \frac{V_m}{\omega L} \sin(\omega t)$$

If  $\phi = \phi_m \sin(\omega t)$

$$v = N \phi_m 2\pi f \cos(\omega t)$$

$$V_m = N \phi_m (2\pi f)$$

$$V_{rms} = \frac{2\pi f N \phi_m}{\sqrt{2}} = 4.44 f N \phi$$

## Ideal Transformers


No core losses

No leakage flux

$$Q \rightarrow 0 \Rightarrow$$

No copper losses

Core does not saturate

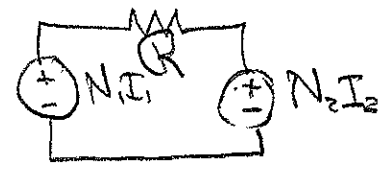


$$\vec{B} = \mu \vec{H}$$


22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



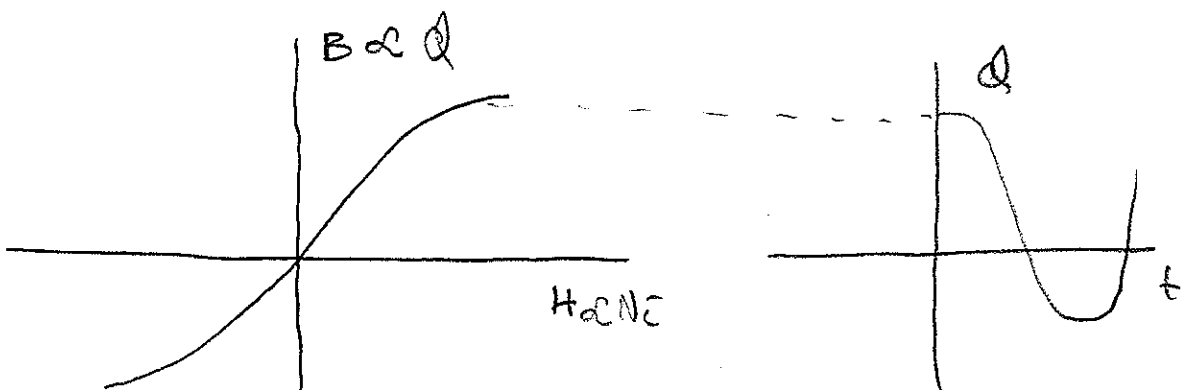
22-141 50 SHEETS  
 22-142 100 SHEETS  
 22-144 200 SHEETS  
 CAMPAC



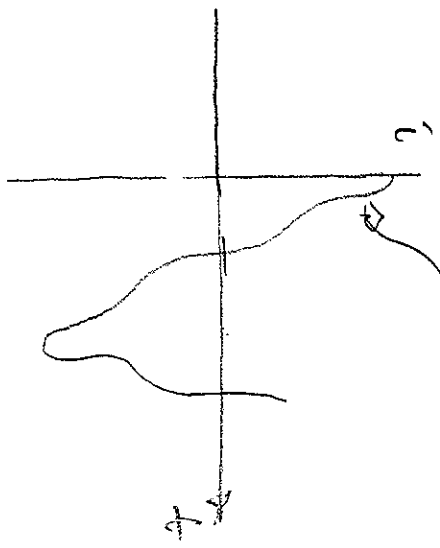
This implies a non sinusoidal current for a sinusoidal voltage.



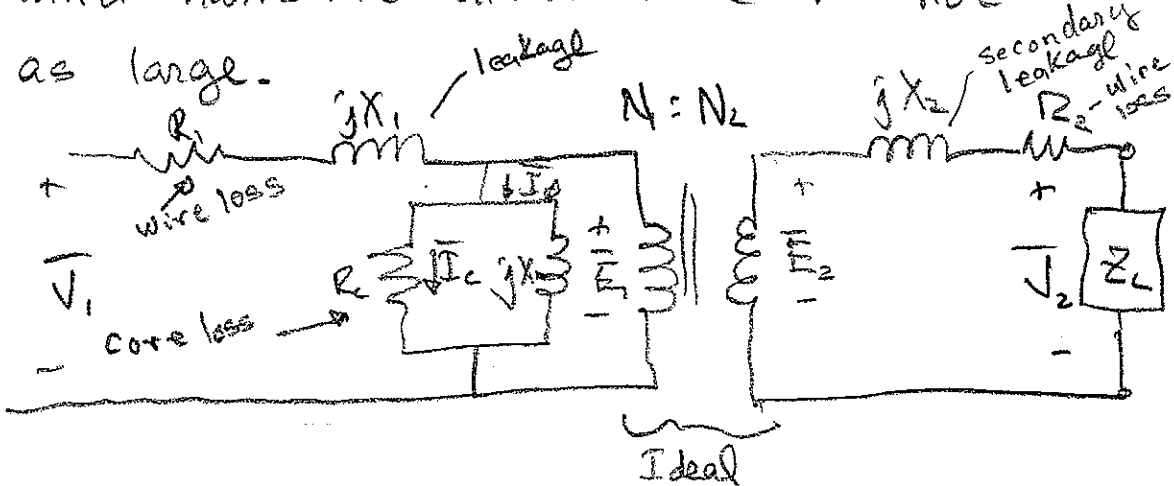If we have a load the back flux reduces the peak flux so that the third harmonic distortion is not as large.




$$\frac{N_1}{N_2} \equiv a$$

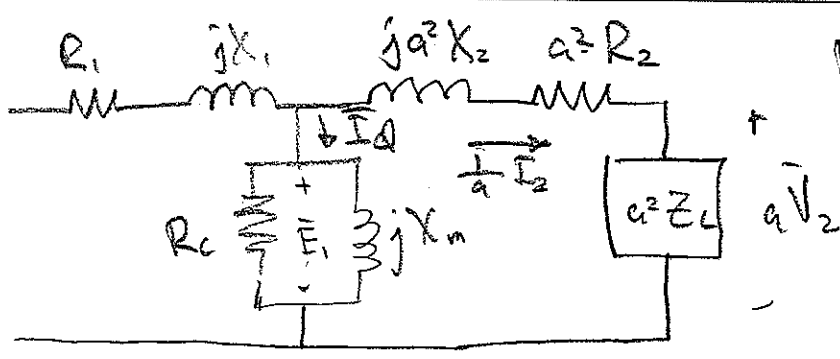

Move to primary.  
 $V_{01}$  can move  
 to secondary  
 as well.

Because  $|(R_1 + jX_1)| \ll |R_c || jX_m|$   
 approximately:

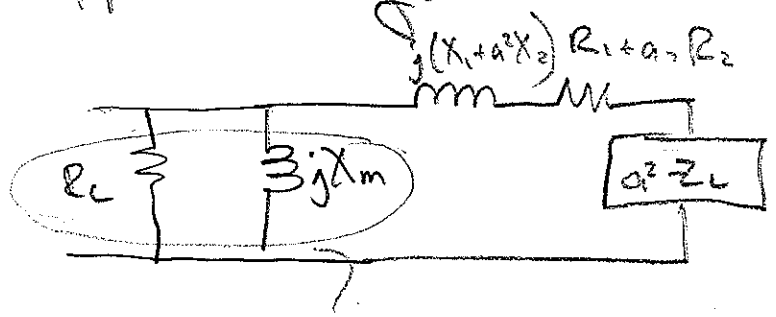

this is  
 OK for  $Z_L$   
 fairly large  
 😊

Sometimes these are ignored as well.

Rod did 4.11 & 4.17.

$$\text{Voltage Regulation} = \frac{V_{2NL} - V_{2FL}}{V_{2FL}} \times 100\%$$

Rod did an example computing the model parameters from open & short circuit tests. He used the approximate model 😊 above. See page 232 & following in text.


Rod did 4.8. Book assumes sc test on the high voltage side. We didn't do that in lab.

Rod does example just like lab analysis in class. He always uses 😊 now.


It is easier to assume the secondary is

operating at rated load.



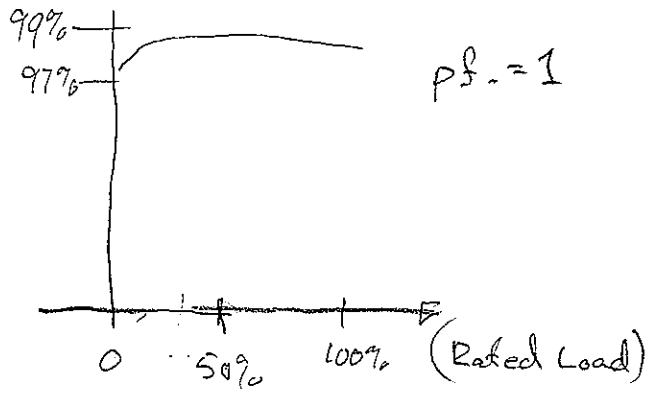
What happens to efficiency as the load decreases?



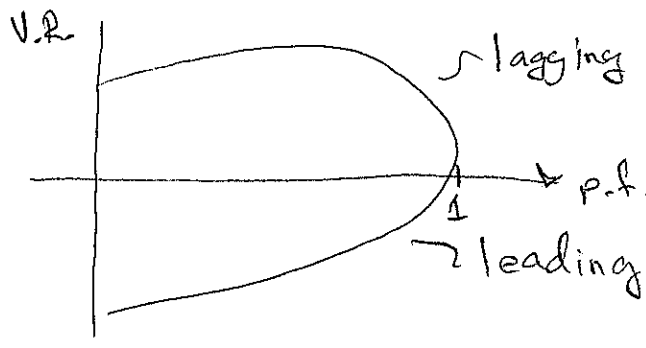Rated Load VR  
 pf = 1, 1.25%  
 pf = 0.8 lag, 2.1%  
 pf = 0.8 lead, -0.83%



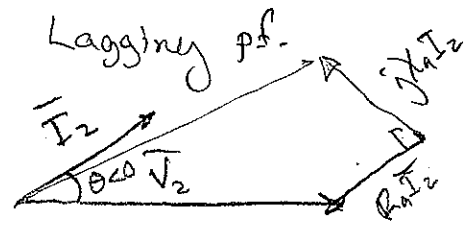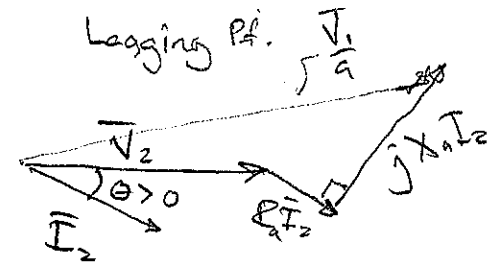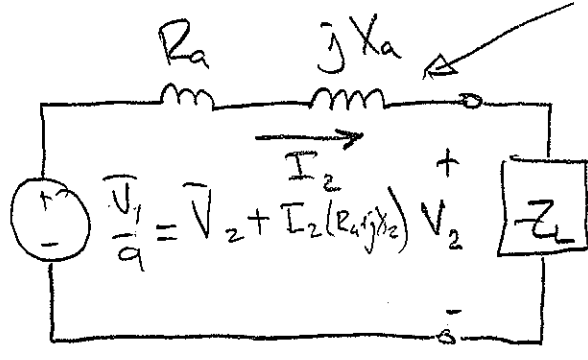Thevenin Equivalent of Transformer & source




=> Negative voltage regulation

Induction Motors are really transformer.  
 Rod did several practice exam problems.  
 The exam is next day.

# Transformers in Three Phase

Y-Y, Δ-Δ, Y-Δ, Δ-Y

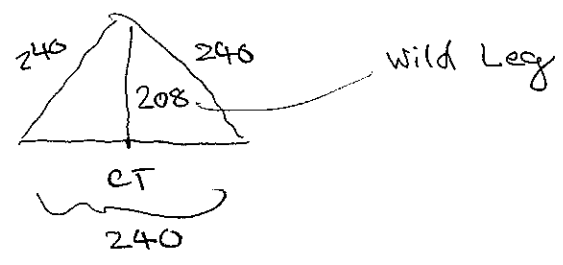

22-141 50 SHEETS  
 22-142 100 SHEETS  
 22-144 200 SHEETS  
 AMPAD

$V I C R \theta$   $\rightleftharpoons$  Electrical System  $\xrightarrow{\text{loss}}$  Mechanical Syst.  $\xrightarrow{\text{loss}}$

$W_e = \int v i dt$

Motor  $\xrightarrow{\text{Field}}$  Generator

$$dW_m = F dx \quad \frac{dW}{dt} = p = F \frac{dx}{dt} = Fv$$

$$dW_m = T d\theta \quad \frac{dW}{dt} = T \frac{d\theta}{dt} = Tw$$

$p = Tw$   
or  $v i$

$$v = N \frac{d\phi}{dt} = L \frac{di}{dt} \quad v = \frac{d\lambda}{dt} \quad (\lambda = Li)$$

if L doesn't change

L changes as the magnetic circuit changes  
 so  $v = \frac{d\lambda}{dt}$  is better.

$$W_f = \frac{1}{2} \int \vec{B} \cdot \vec{H} d\tau = \int_0^t \frac{d\lambda}{dt} i dt = \int_0^t i \frac{d(Li)}{dt} dt$$

$$= \frac{1}{2} Li^2 \text{ if } L \text{ doesn't change}$$

Electrical energy = Mechanical Energy + Field Energy

$$dW_e = dW_m + dW_f$$

$$dW_e = v i dt = i \frac{d\lambda}{dt} dt = i d\lambda$$

$$dW_f = dW_e - dW_m$$


$$dW_f = i d\lambda - T d\theta$$

Blocked Rotor

$$dW_f = i d\lambda$$

$$N\Phi = \lambda$$
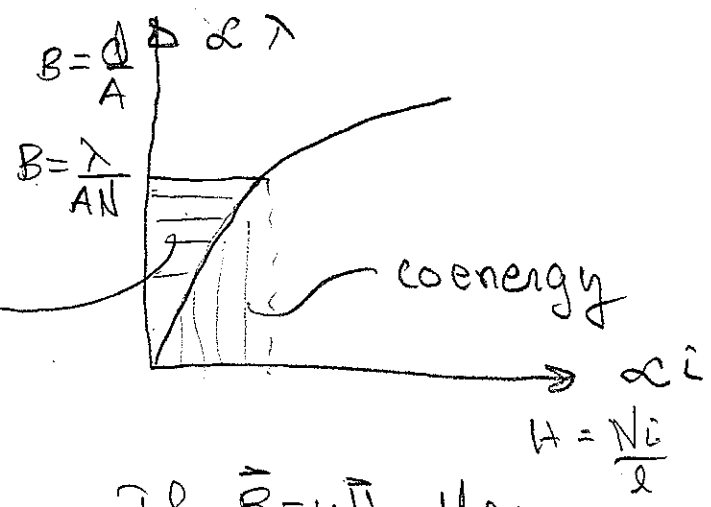
$$W_f = \int \vec{B} \cdot \vec{H} dV = \int i d\lambda$$



$$W_f = \lambda i - \underbrace{\int \lambda di}_{\text{coenergy}}$$

If  $\vec{B} = \mu \vec{H}$  then the energy in the field is equal to the co-energy.

$$W_f = \int i d\lambda = \int i d(N\Phi)$$

$$= \int N i d\Phi = \int \underbrace{\frac{N^2}{\mu R}}_{\text{MMF}} d\Phi = \int \frac{N^2}{R} d\left(\frac{\mu \Phi}{N}\right) = \frac{1}{2} \frac{\mu^2 \Phi^2}{R}$$

$$= \int R \Phi d\Phi = \frac{1}{2} R \Phi^2 \quad \Phi = Ni = R\Phi$$

$$dW_f = dW_e - dW_m$$


$$\frac{dW_f}{dt} = \frac{dW_e}{dt} - \frac{dW_m}{dt} \quad W_f = f(\lambda, \theta) \text{ or } W_f(\lambda, x)$$

$v_i$                        $T\omega$  or  $F_x v_x$

$$\frac{dW_e}{dt} = \underbrace{\frac{dW_e}{d\lambda} \frac{d\lambda}{dt}}_{i \frac{d\lambda}{dt}} + \underbrace{\frac{dW_e}{d\theta} \frac{d\theta}{dt}}_{-T\omega}$$

$$\text{So } i = \frac{dW_f}{d\lambda} \quad \& \quad T = -\frac{dW_f}{d\theta}$$


$$\text{or } F = -\frac{dW_f}{dx}$$

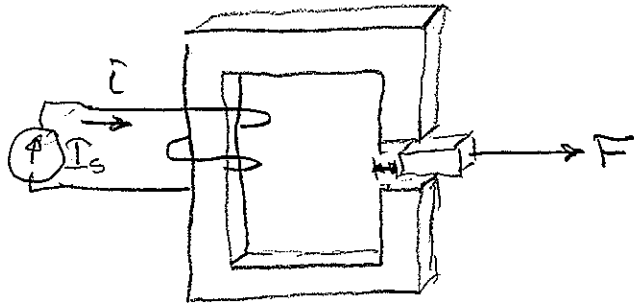

Use "virtual work".

$$W = \int i d(Li) = i^2 L$$

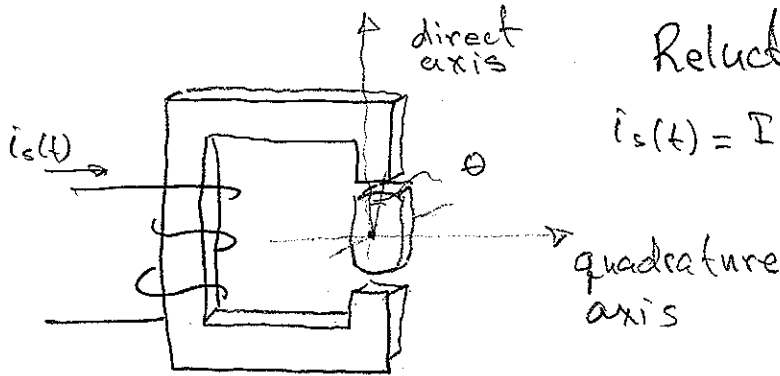
22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



### Reluctance Motors


$$i_s(t) = I_s \sin(\omega t)$$

$$R = \frac{l}{\mu A}$$

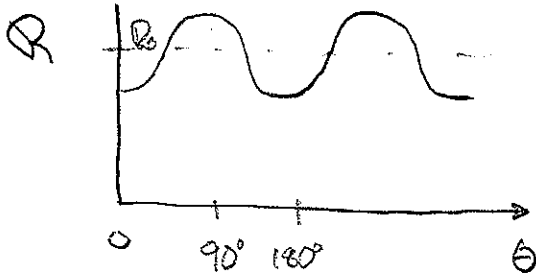

$$R_0 \approx R_0 - R_1 \cos(2\theta)$$

$$L = \frac{N^2}{R}$$

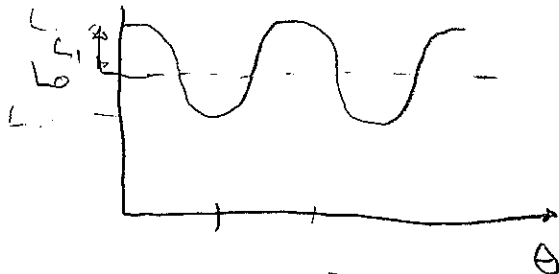

$$L = L_0 + L_1 \cos(2\theta)$$

$$T = -\frac{dW_f}{d\theta}$$

$$W_f = \int i d(Li) \Rightarrow \frac{dW_f}{d\theta} = \frac{i d(Li)}{d\theta}$$

$$= i^2 \frac{dL}{d\theta} + iL \frac{di}{d\theta}$$

$$\theta = \omega_m t + \delta$$

$$T = -\frac{dW_f}{d\theta} = -i^2 \frac{dL}{d\theta} - \cancel{iL \frac{di}{d\theta}}$$

} Rod didn't do this. I did. Rod used  $\frac{1}{2} Li^2$   
 got  $\langle T \rangle = -\frac{I_s^2 L_1}{4} \sin(2\delta)$

$$\begin{aligned}
 T &= + I_s^2 \sin^2(\omega t) L_2 \sin(2\theta) \\
 &= + 2 I_s^2 \sin^2(\omega t) \sin(2(\omega t + \delta)) \\
 &= + 2 L I_s^2 \left( \frac{1 - \cos(2\omega t)}{2} \right) \sin(2(\omega t + \delta)) \\
 &= - L I_s^2 \cos(2\omega t + \delta) - \frac{L I_s^2}{2} (\sin(2\omega t - 2\omega_m t - 2\delta) + \sin(2\omega t + 2\omega_m t + 2\delta))
 \end{aligned}$$

$\langle T \rangle = -\frac{L I_s^2}{2} \sin(-2\delta)$  when  $\omega_m = \omega$ .

Otherwise  $\langle T \rangle = 0$ .

$\delta_{max} = 45^\circ$


So the factor of two remains in the difference.

Why do we do all the current source excited examples?



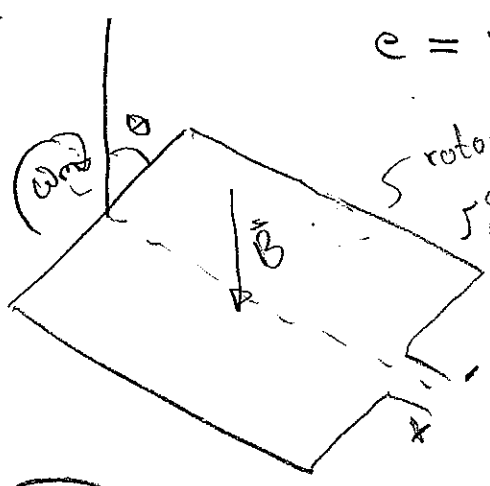
### DC Generator Basics

$$\begin{aligned}
 \phi &= BA \sin \theta = BA \sin(\omega t) \\
 e &= N \frac{d\phi}{dt} = NBA \omega_m \cos(\omega t)
 \end{aligned}$$



rotor armature  $\vec{F}_e = q \vec{v} \times \vec{B}$   
 (where potential is induced)  $\phi = BA$



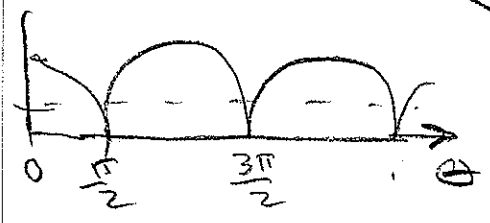
Apply slip rings to get a rectified output



$\langle e \rangle = \frac{2N\phi\omega_m}{\pi}$



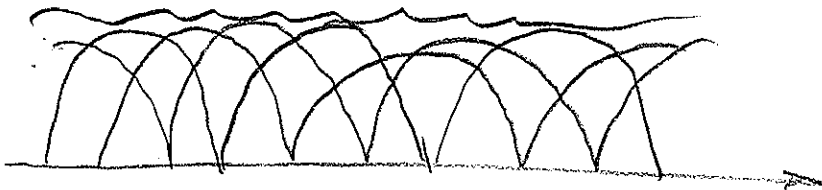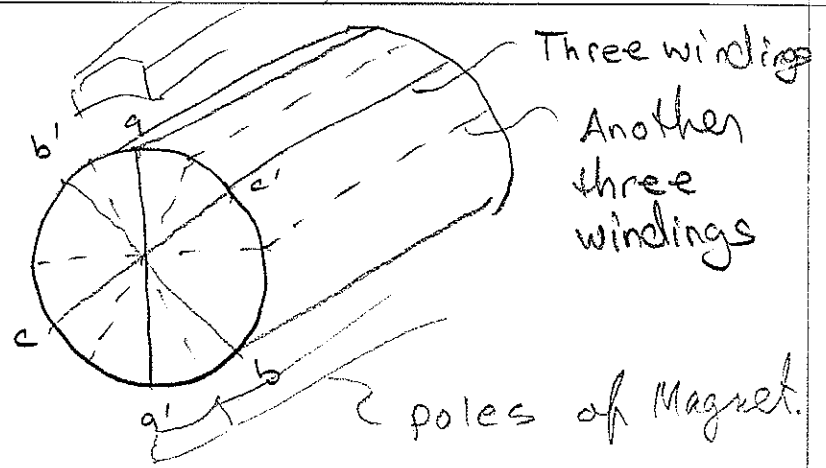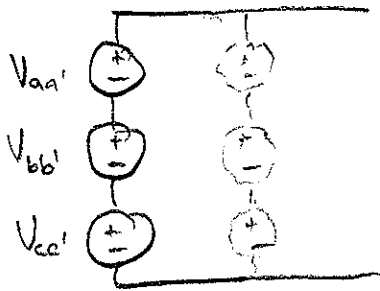22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



$N \equiv$  Number of turns

$Z \equiv$  " " conductors

$a \equiv$  " " parallel paths

$\langle e \rangle \equiv E_a = \frac{Z \Phi_d \omega_m p}{a \pi 2} (3) \equiv$  Armature potential

Put another pole pair to double the output.


$p \equiv$  # magnetic poles

$E_a \equiv K_a \Phi_d \omega_m$  where  $K_a = \frac{Z p}{2 a \pi} \equiv$  armature constant


Motor speed Equation

As a motor:

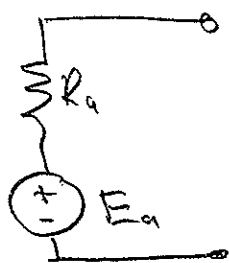$\omega_m = \frac{E_a}{K_a \Phi_d}$  Run away motor.



Armature Model


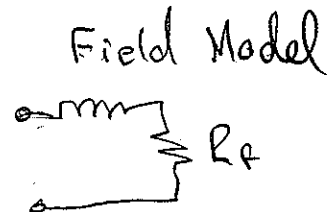


Field Model


22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS  
GAMPAD

In motors the armature reaction causes the speed to increase under load.


### Separately Excited Generator

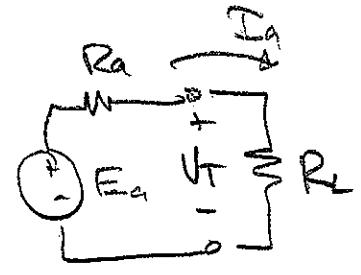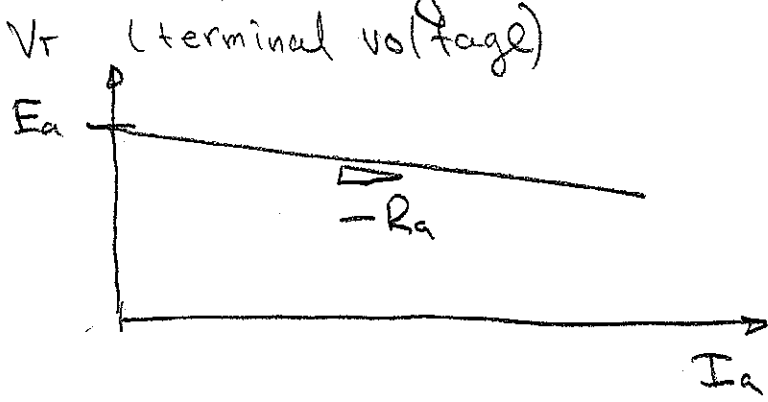


Motor  
Current changes direction.

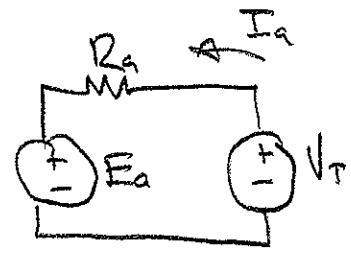


$R_a$  includes series field, etc.

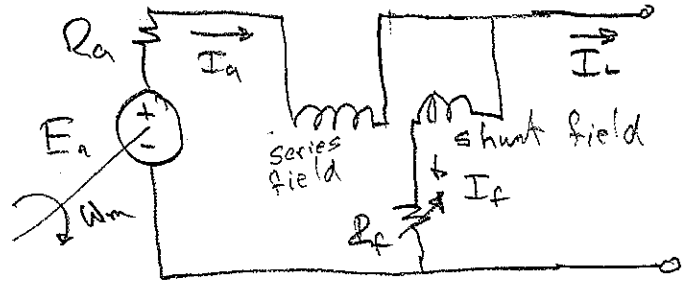



self excited  
Generator

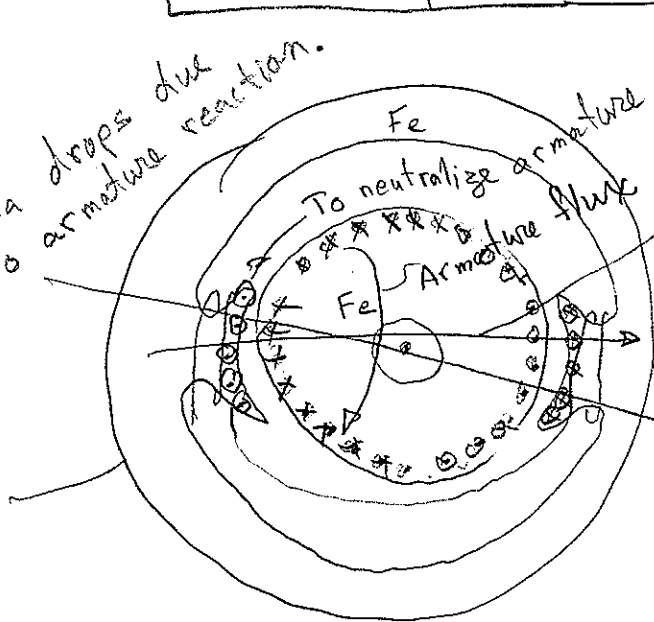

$E_a$  drops due to armature reaction.

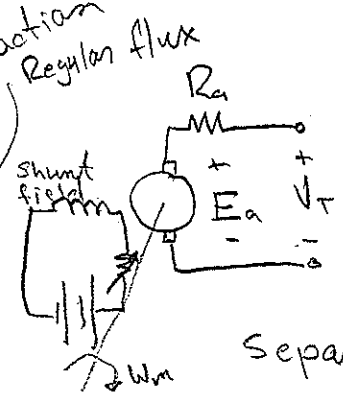


Separately  
Excited  
self Excited

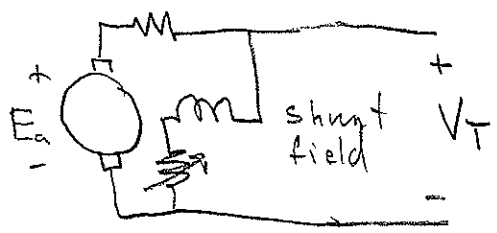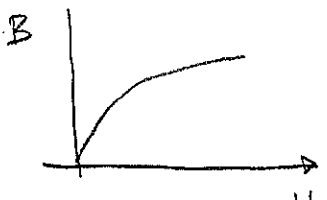


⇒ Reduced direct axis flux due to Armature flux reaction. The more armature current you draw the lower the

# Compound Self Excited Motor



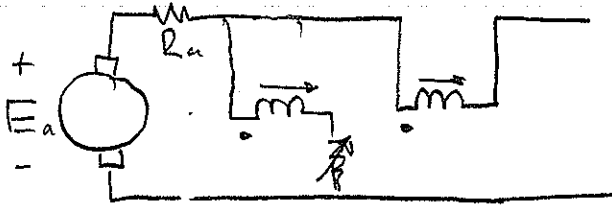


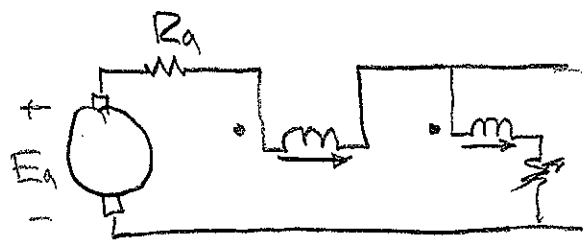Short Shunt Cumulatively Compound Generator  
 You can do a Differential Compound Generator but it has poor voltage regulation.



Long Shunt Cumulatively Compound Generator

## Commutator

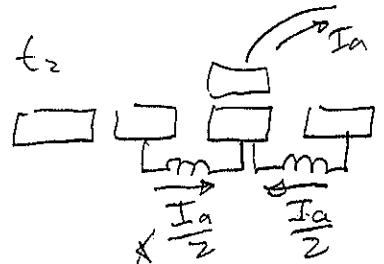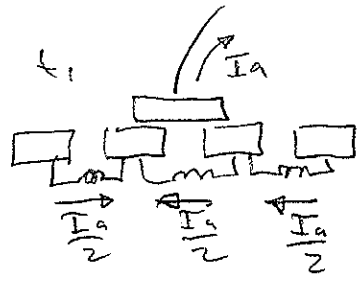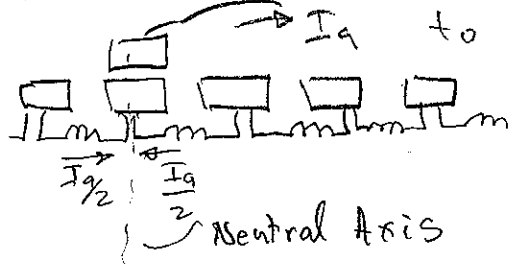


Somewhat adding the commutating poles induces a voltage that counteracts the induced voltage from switching.

This suddenly changed directions  
 $v = L \frac{di}{dt} \Rightarrow$  arcing + pitted

22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



No Load  $\omega_m = \text{constant}$

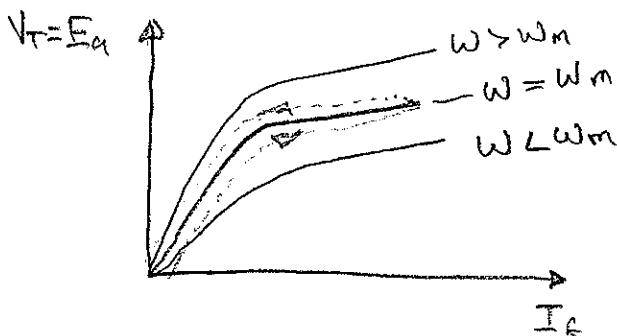

Easy to measure.


$$E_{a1} = K_a \Phi \omega_{m1}$$

$$E_{a2} = K_a \Phi \omega_{m2}$$


Magnetization Curve

$$\frac{E_{a1}}{E_{a2}} = \frac{\omega_{m1}}{\omega_{m2}}$$


Commutator losses about 2V across them.

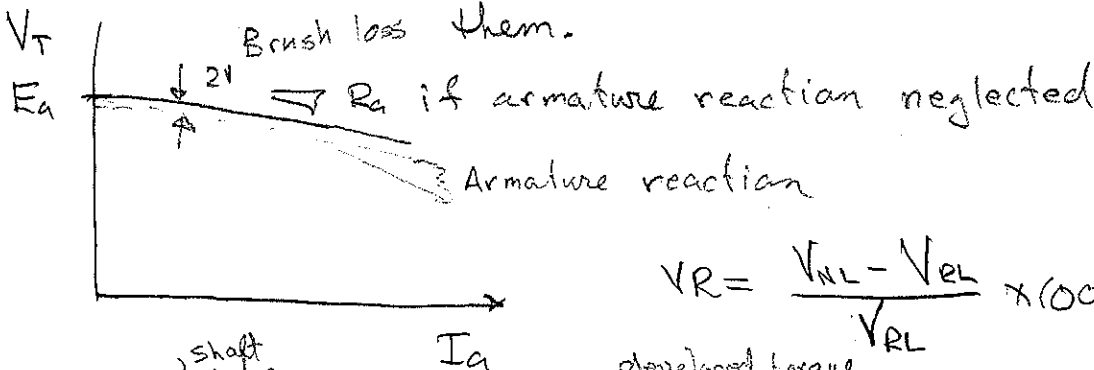
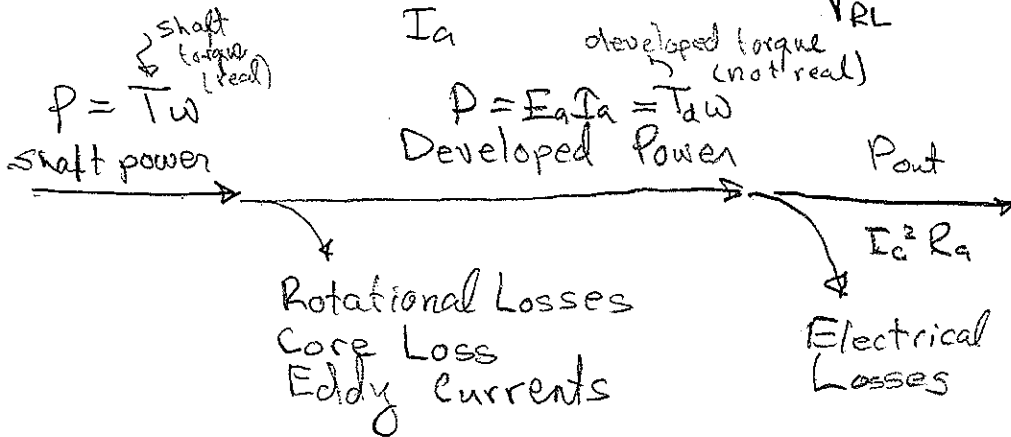
$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$




Self Excited D.C. Generators

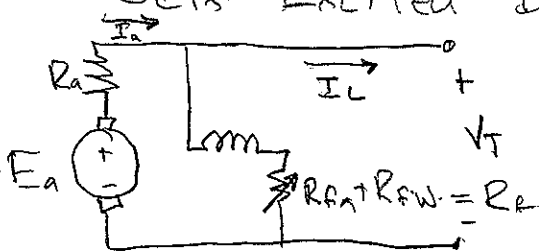



$$I_f = \frac{E_a}{R_f + R_{fw}}$$

No Load

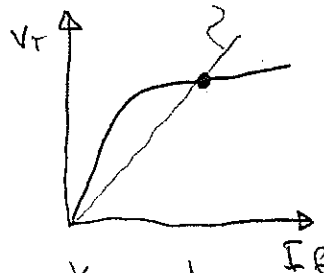

Based on residual flux.



Only works when residual flux is aiding.

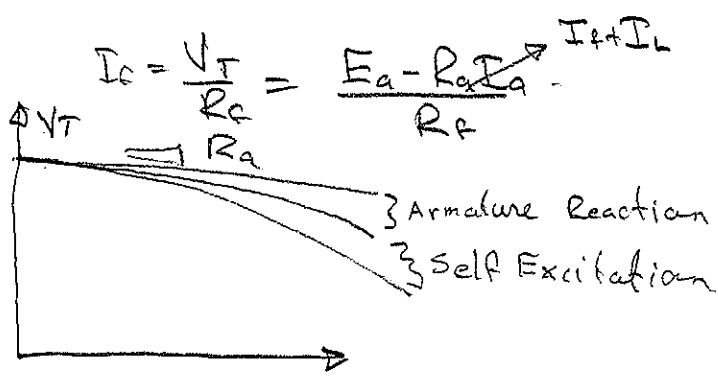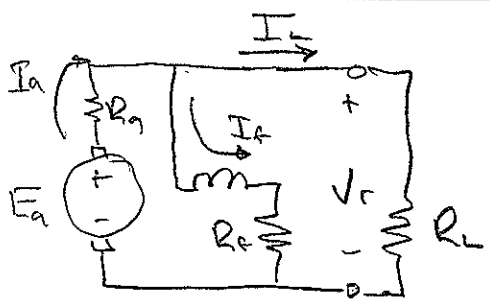

$$E_a = k_a \phi \omega_m$$

Rod did Example 5.6

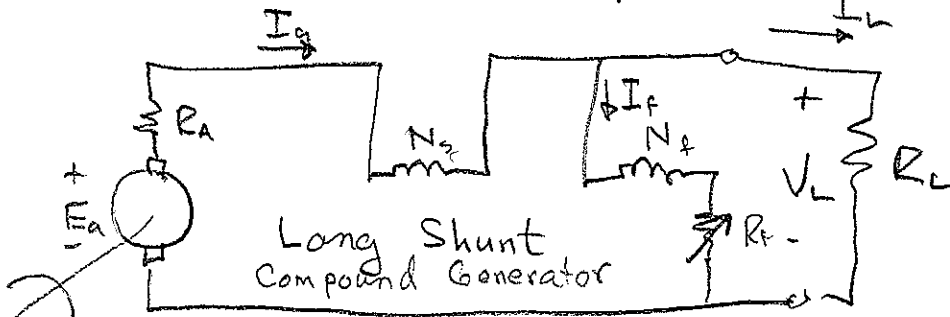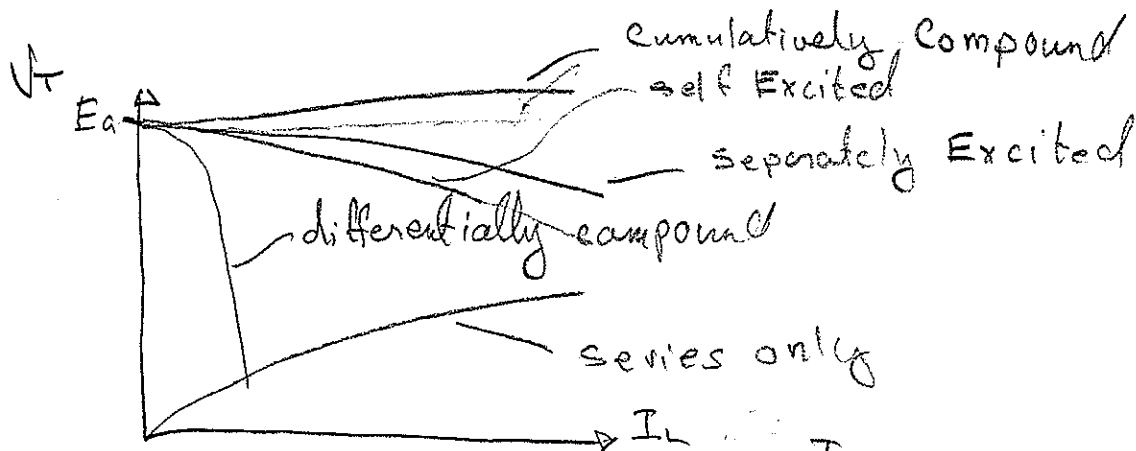To measure Protational loss drive the machine as a motor &  $P_{in} = P_{Loss}$  assuming there is no mechanical load.



$$P_d = T_d \omega_m = E_a I_a \quad E_a = k_a \phi \omega_m$$

$$\Rightarrow T_d = k_a \phi I_a$$


Rod did an example designing a series winding to produce flat regulation

22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS



Rod did #42 as an example.

Shunt Field

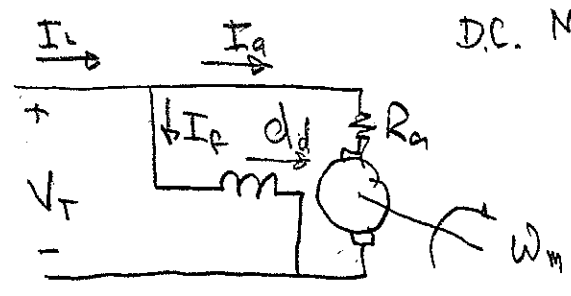



$$E_a = K_a \phi_d \omega_m$$

$$E_a = V_T - I_a R_a = K_a \phi_d \omega_m$$

$$T_d = k_t \phi_d I_a \Rightarrow I_a = \frac{T_d}{k_t \phi_d}$$

$$I_a E_a = T_d \omega_m$$
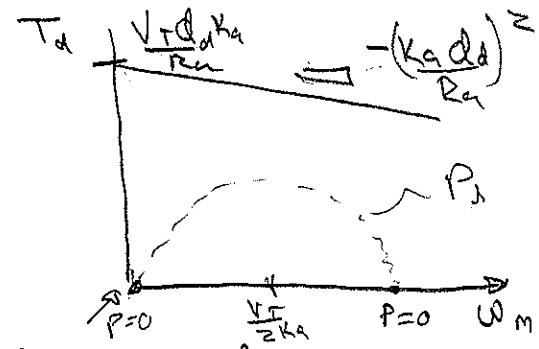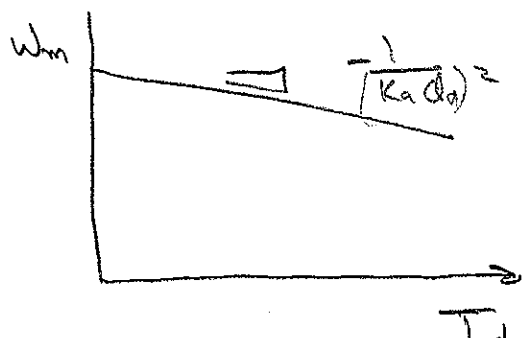
$$\omega_m = \frac{V_T}{K_a \phi_d} - \frac{I_a R_a}{K_a \phi_d} = \frac{V_T}{K_a \phi_d} - \frac{T_d R_a}{(K_a \phi_d)^2}$$



$$T_d = - \left( \omega_m - \frac{V_T}{K_a \phi_d} \right) \frac{K_a^2 \phi_d^2}{R_a} = - \frac{K_a^2 \phi_d^2}{R_a} \omega_m + \frac{V_T K_a \phi_d}{R_a}$$

$$P_d = T_d \omega_m = \frac{V_T K_a \phi_d}{R_a} \omega_m - \frac{K_a^2 \phi_d^2}{R_a} \omega_m^2$$

$P_d = 0$  when  $\omega_m = 0$  + when  $\omega_m = \frac{V_T}{K_a \phi_d}$


Find where in  $\omega_m$ ,  $P_d$  is max.

$$\frac{dP_d}{d\omega_m} = 0 \Rightarrow \omega_m = \frac{V_T}{2 K_a \phi_d}$$

$$P_{d,max} = \frac{V_T^2}{2 R_a} - \frac{K_a^2 \phi_d^2}{R_a} \frac{V_T^2}{4 K_a^2 \phi_d^2} = \frac{V_T^2}{4 R_a}$$

Watch out for starting current.  
 " " " losing flux.

# Series Field DC Motor

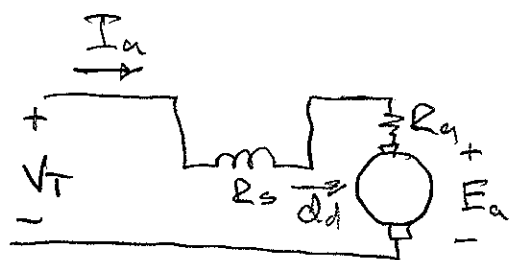

$$E_a = V_T - I_a(R_a + R_s)$$

$$= K_a \phi \omega_m$$

$$\phi = I_a N_s = R \phi$$

$$\omega_m = \frac{V_T - I_a(R_a + R_s)}{K_a \phi} = \frac{V_T}{K_a \phi} - \frac{I_a(R_a + R_s)}{K_a \phi}$$


$$= \frac{V_T}{K_a \phi} - \frac{R(R_a + R_s)}{K_a N_s}$$

constant

$$\frac{R}{N_s} = \frac{I_a}{\phi}$$

$$T_a = K_a \phi I_a = \frac{K_a R}{N_s} \phi^2$$
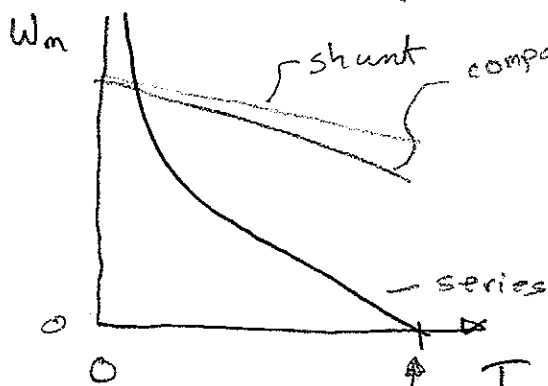
$$\text{so } \phi = \sqrt{\frac{N_s T_a}{K_a R}} \Rightarrow \omega_m = \frac{V_T}{K_a \sqrt{T_a}} \sqrt{\frac{R}{N_s}} - \frac{R(R_a + R_s)}{K_a N_s}$$




Unloaded, the series motor runs away. Great starting torque.


$$T_d = \frac{K_a V_T^2 N_s}{R(R_a + R_s)}$$
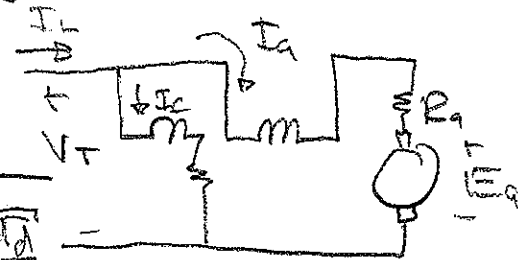
## Compound Motor

$$\omega_m = \frac{V_T}{K_a \left[ \frac{N_s I_f}{2R} + \sqrt{\left( \frac{N_s I_f}{2R} \right)^2 + \frac{N_s T_d}{R K_a}} \right]}$$

$$- \frac{T_d(R_a + R_s)}{K_a \left[ 2 \left( \frac{N_s I_f}{2R} \right)^2 + \frac{N_s T_d}{R K_a} + \frac{N_s I_f}{R} \sqrt{\left( \frac{N_s I_f}{2R} + \frac{N_s T_d}{R K_a} \right)} \right]}$$



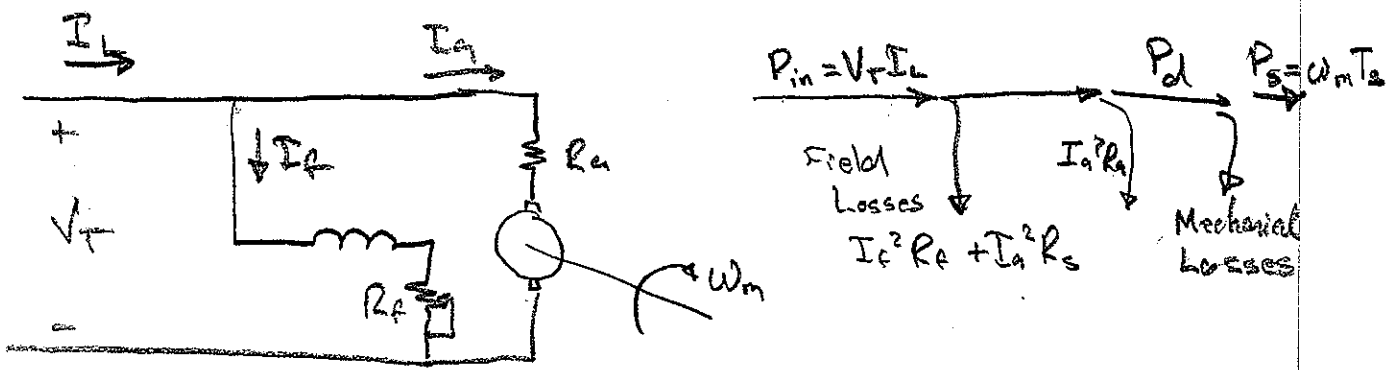

$$E_a = K_a \phi \omega_m$$

$$\eta = \frac{P_s}{P_{in}}$$

$$P_d = E_a I_a$$

$$T_d = \frac{P_d}{\omega_m} = \frac{K_a \phi \omega_m I_a}{\omega_m}$$

Rod did an example finding  $\eta$ ,  $\omega_{FL}$ .  
 Rod did another example with magnetization curve & armature reaction (and without AR)


$$I_{sc} = I_f - \frac{K_a \phi I_a}{N_f}$$

$$\phi = N_f I_f - K_a I_a$$

Armature reaction

Rod did another example with a cumulatively compound motor short shunt.

Rod did 6.23 from the book.

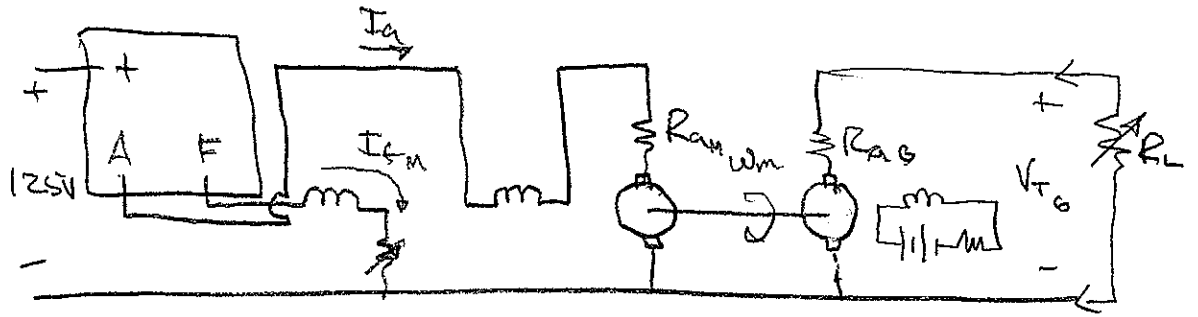


### DC Motor Lab

Resistor limits start up current. → slowly move to on.  
 solenoid holds it on




Rod did a series motor example.


### Induction Motors

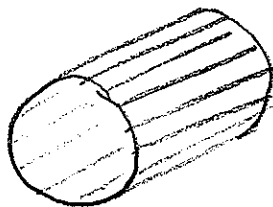

Squirrel Cage Rotor

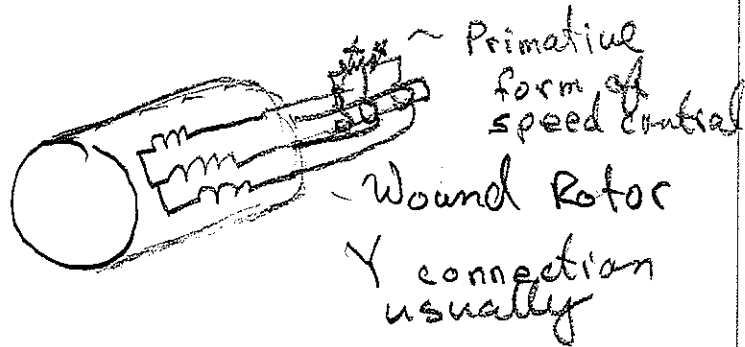

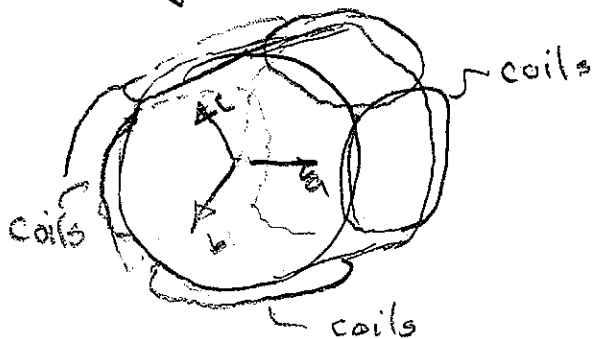Armature is fixed with a rotating magnetic field.



$$i_a = NI \cos(\omega t)$$

$$i_b = NI \cos(\omega t - 120^\circ)$$


$$i_c = NI \cos(\omega t - 240^\circ)$$

$$\vec{F} = i_a \hat{a} + i_b \left(\frac{1}{2} \hat{a} + \frac{\sqrt{3}}{2} \hat{b}\right) + i_c \left(-\frac{1}{2} \hat{a} + \frac{\sqrt{3}}{2} \hat{b}\right)$$

$$\vec{F} = NI \left\{ \left[ \cos(\omega t) - \frac{1}{2} \cos(\omega t - 120^\circ) - \frac{1}{2} \cos(\omega t - 240^\circ) \right] \hat{a} + \left[ \frac{\sqrt{3}}{2} \cos(\omega t - 120^\circ) + \frac{\sqrt{3}}{2} \cos(\omega t - 240^\circ) \right] \hat{b} \right\}$$

$$\cos(a-b) = \cos a \cos b + \sin a \sin b$$

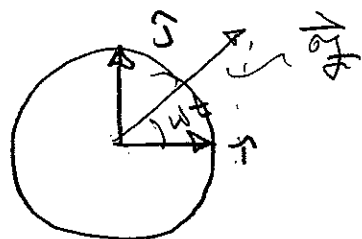
$$\vec{F} = \frac{3}{2} \left[ \cos \omega t \hat{a} + \sin(\omega t) \hat{b} \right] NI$$



$n_s \equiv$  stator field's speed  
 $n_s = 60 f = \frac{60 \omega}{2\pi}$  RPM  
 For two poles/phase

In general  $n_s = \frac{120f}{P}$  where  
 $P$  is the number of poles/phase.

$n$	$n_s$
2	3600
4	1800
6	1200
∞	900

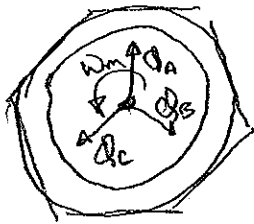

Subscript 1  $\Rightarrow$  Stator

" 2  $\Rightarrow$  Rotor

$n_m \equiv$  mechanical speed

Assume  $n_m = 0$  (blocked rotor or open rotor windings)

$$\phi_{A1} = \phi_m \sin(\omega t)$$

$$\phi_2 = k_2 \phi_m \sin(\omega t)$$

$$e_2(t) = N \frac{d\phi_2}{dt} = 2\pi f_1 N_2 k_2 \phi_m \cos(\omega t)$$

$k_2$  is fraction of flux going through the rotor

$$\text{rms } E_2 = \frac{2\pi f_1 N_2 k_2 \phi_m}{\sqrt{2}} = 4.44 f_1 N_2 \phi_m$$

$$\text{rms } E_1 = 4.44 f_1 N_1 k_2 \phi_m \quad (\text{back emf})$$

$$\frac{E_1}{E_2} = \frac{k_1 N_1}{k_2 N_2} \approx \frac{N_1}{N_2} = a$$

Like a transformer with an airgap.

$$n_s = \frac{120f}{P} \quad (\text{RPM}) \quad f_1 = \frac{P}{120} n_s$$

$$s \equiv \text{slip} \equiv \frac{n_s - n_m}{n_s} \leq 1 \quad |z s > 0$$

$$n_m = (1-s)n_s$$

$$f_2 = \frac{P}{120} (n_s - n_m) = \frac{P}{120} s n_s$$

$$f_2 = \frac{P}{120} s \left(\frac{120}{P}\right) f_1 = s f_1$$

The frequency on the secondary is different than the frequency on the primary.

$s = 1 \Rightarrow$  blocked rotor

$$E_r = 4.44 s f_1 N_2 k_2 \Phi_m \quad \leftarrow \text{rotating rotor (rms)}$$


$$= s E_2$$

$n_{rf} \equiv$  speed of rotor field  $= n_m + n_2$

$$n_{rf} = n_s(1-s) + n_2$$

$$n_2 = 60 f_2 = 60 s f_1 = s n_1 = s n_s$$

$$n_{rf} = n_s(1-s) + s n_s = n_s$$

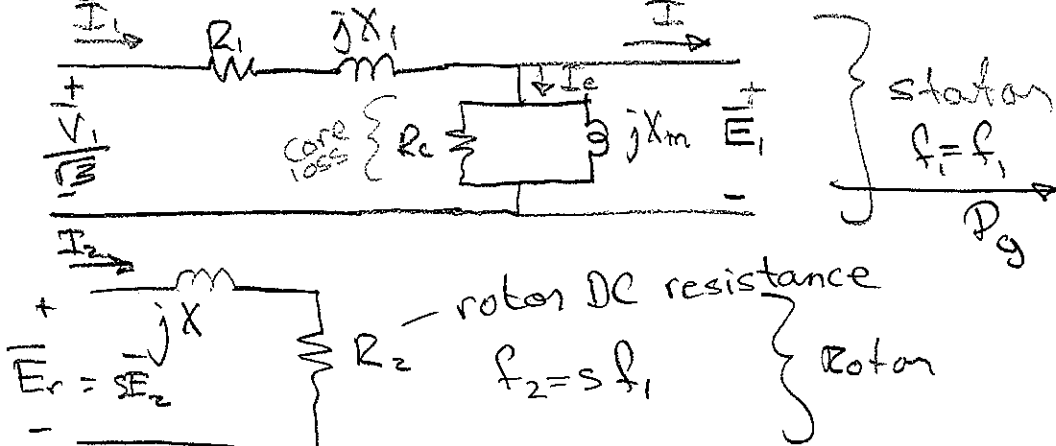


$$jX = j2\pi s f_1 L = j s X_2$$

$$\vec{I}_2 = \frac{s \vec{E}_2}{R_2 + j s X_2}$$

$$\vec{I}_2 = \frac{\vec{E}_2}{\frac{R_2}{s} + j X_2}$$

$$P_{3cu} = 3 I_2^2 R_2$$

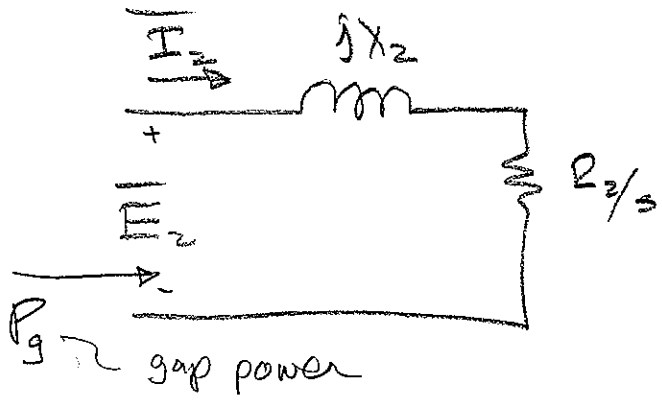


$E_2$  is at  $f_1$   
 so this is combinable with the primary, by multiplying by  $a^2$ .



$$P = 3I_2^2 R_{2/s}$$


Cu loss & mechanical power.
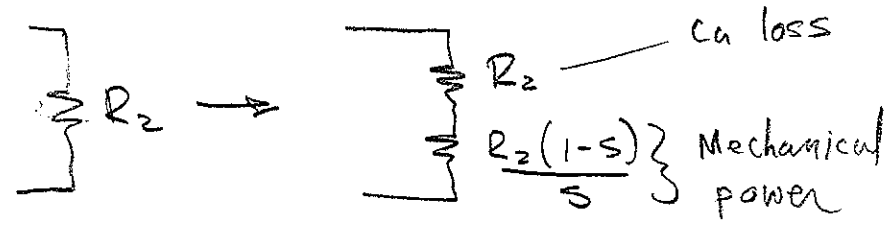
$$\frac{R_2}{s} = R_2 + \frac{R_2}{s}(1-s)$$



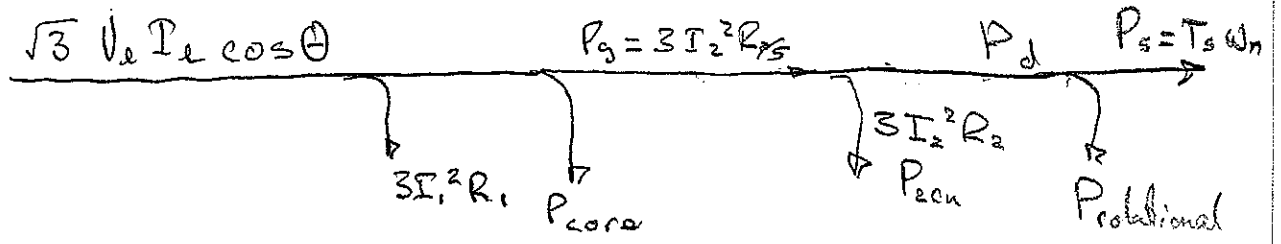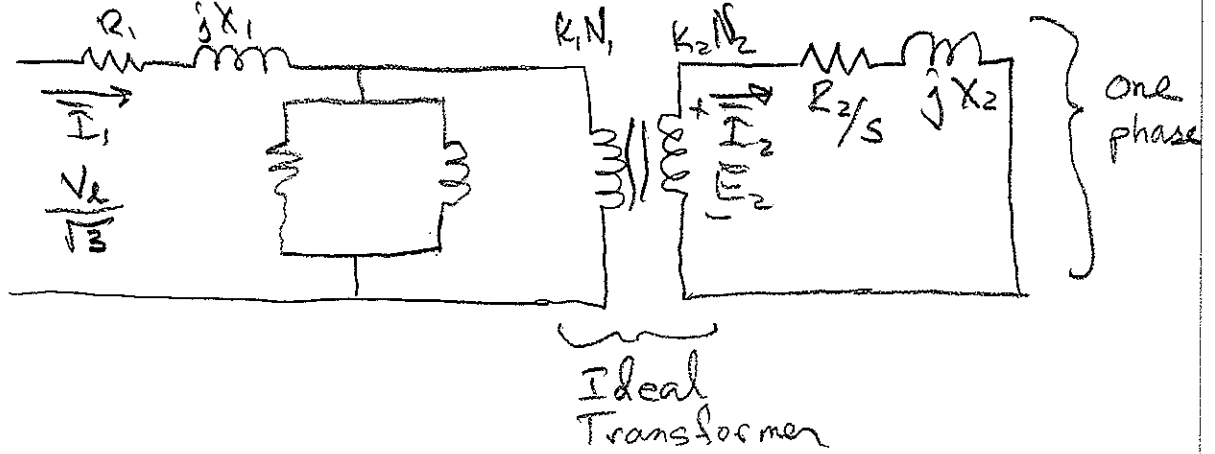Put it all together now that the frequencies are the same.



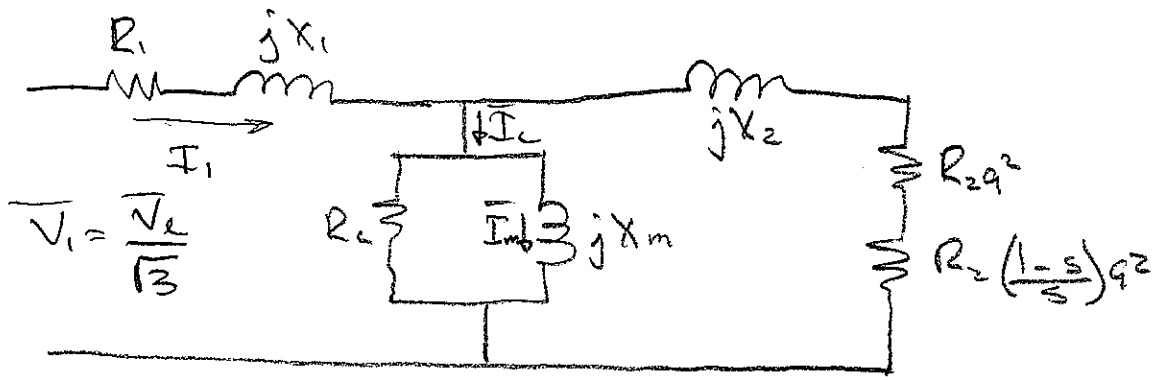


$R_c \gg X_m$  so often it is ignored.

Rod did an example.  
Rod did example 9.7 & 9.8.

Synchronous Machines (Chapter 8)  
The armature is the same as an induction motor. The rotor is an electromagnet. AC is generated via synchronous generators (alternators).

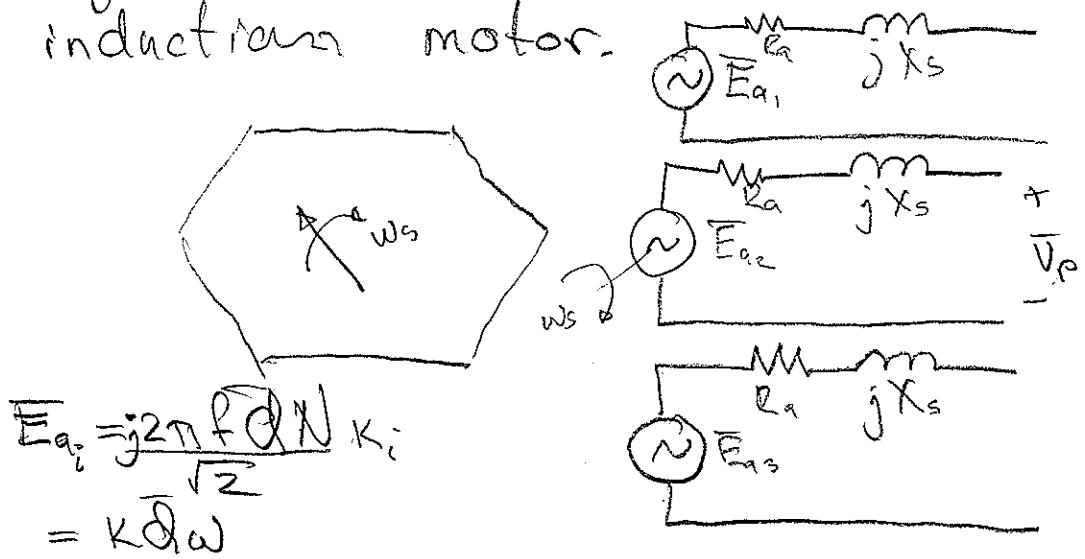Look up three phase rectifiers  
Magneto has a permanent magnet rotor.  
Synchronous motor is started as an induction motor.



22-141 50 SHEETS  
 22-142 100 SHEETS  
 22-144 200 SHEETS  
 AMPAC

22-141 50 SHEETS  
22-142 100 SHEETS  
22-144 200 SHEETS







$jX_s$  is from leakage reactance & armature reaction

$$E_a = k \Phi \omega$$

Generator action

$$\vec{E}_a = \vec{V}_p + \vec{I}_a (R_a + jX_s)$$

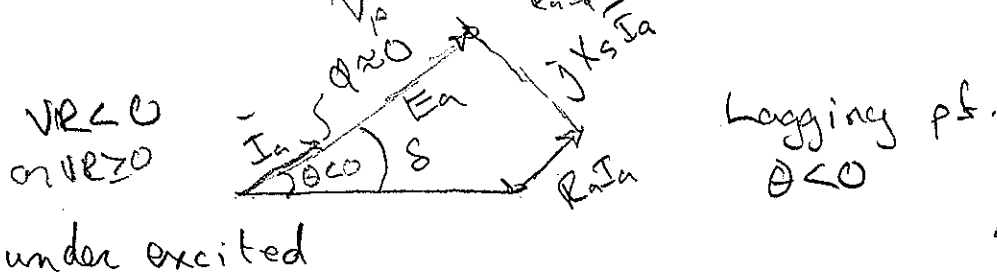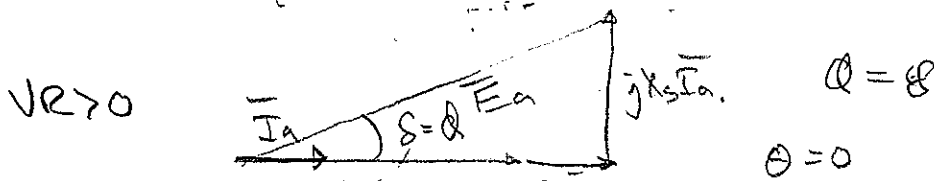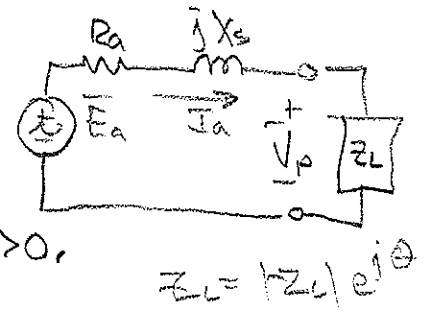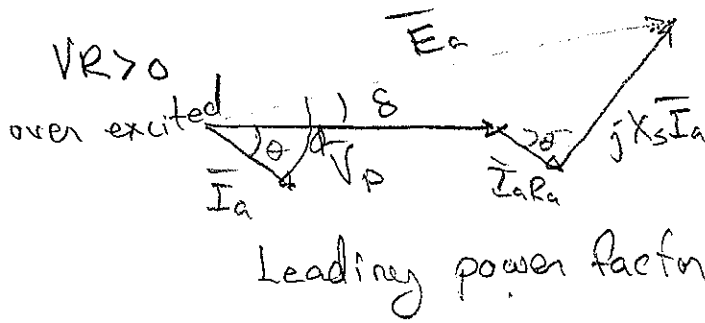Motor Action  $\vec{I}_a$  changes direction.




generator


$V_R \equiv$  voltage regulation.  
 $\theta \equiv$  power factor as seen from  $\vec{E}_a$ .

$$\vec{E}_a = \vec{V}_p - \vec{I}_a (R_a + jX_s)$$


Motor ( $\vec{I}_a$  changes direction)

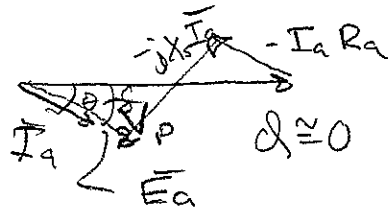

$\theta > 0$   
under excited

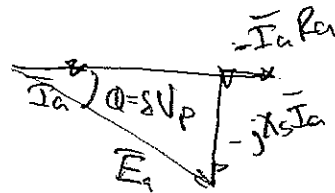

$\theta = 0$

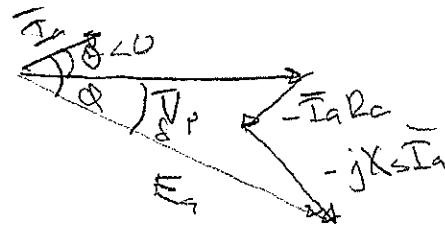

$\theta < 0$   
over excited


We can control the power factor by changing  $\delta$  which changes the length of  $\vec{E}_a$ .

$$P_o = 3 V_p I_L \cos \theta$$


$\vec{I}_L = \vec{I}_a$

$$P_d = 3 V_p I_L \cos \delta$$

Ignore  $\vec{I}_a R_a$ .

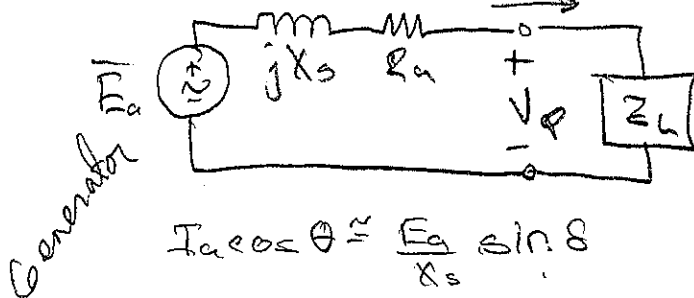

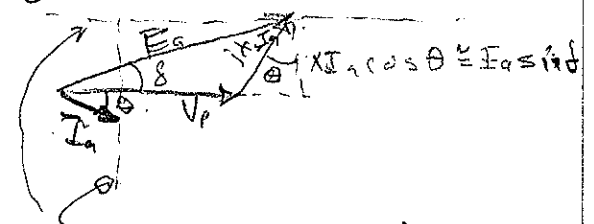
$$I_a \cos \theta \approx \frac{E_a \sin \delta}{X_s}$$



loci of constant power


$E_a = k \omega \Phi_m$   
 $E_a$  doesn't change with  $P_L$

As a motor (ignoring  $\bar{I}_a R_a$ ):

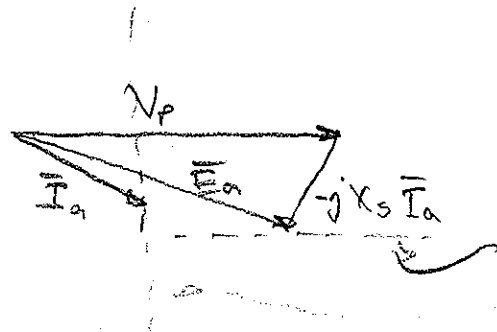

loci of constant power  
change  $\delta$  to move  $\bar{I}_a + \bar{E}_a$  along these loci.

$$P_o = T \omega_s$$

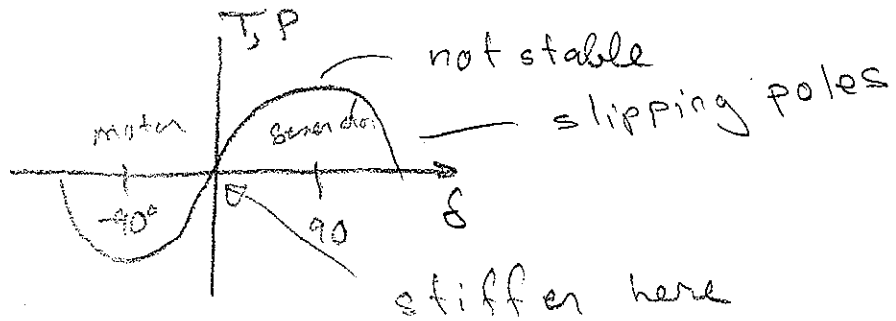

$$P_o = \frac{3V_p E_a \sin \delta}{X_s}$$

$\delta > 0 \Rightarrow$  Generator

$\delta < 0 \Rightarrow$  Motor

$$\text{stiffness} = \frac{dP}{d\delta}$$

Lab machines are 4 pole so strobe shows  $\delta/2$ .

Rod did 8-1 as an example.  
" " 8-5 " " " "




How do we start single phase motors?


1) One way to do it is an auxillary winding. One winding has large  $R$  & small  $X$  and one with small  $r$  & large  $X$ .

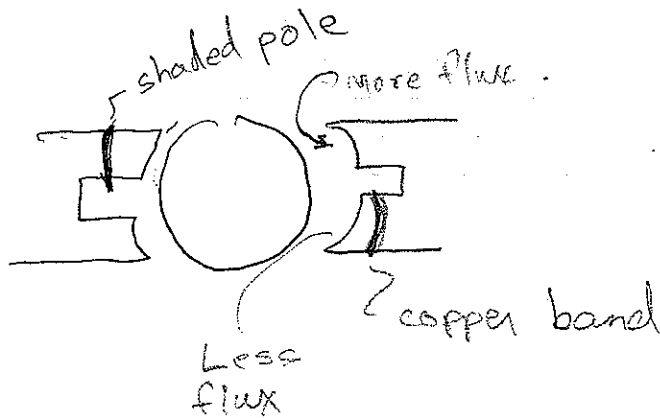2) Use an auxillary winding with a parallel or series capacitor.

You need time & space quadrature. Sometimes you remove the auxillary coil with a centrifugal switch.



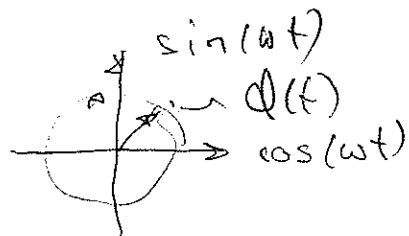Reluctance motors have reluctance that changes as a function of  $\theta$ .



Measure field current on the synchronous machines by using the 10 A scale. Strobes can induce epileptic seizures.