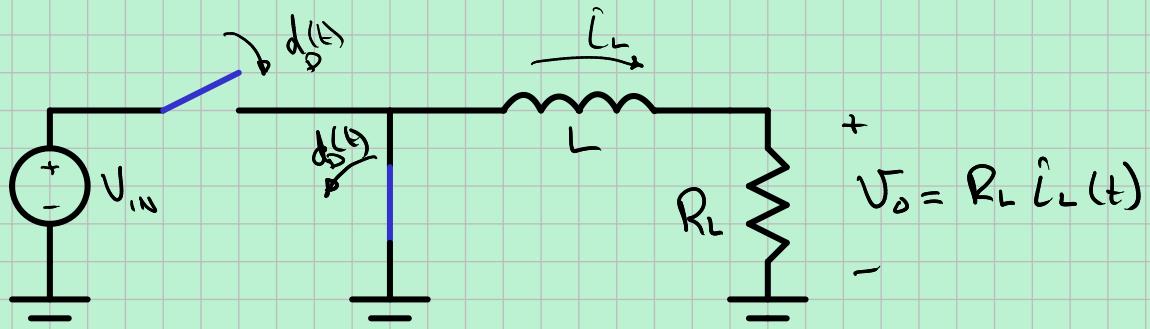


Buck Converter Without an Output Capacitor



$$\text{For } d(t): \quad L \frac{di_L}{dt} = V_{in} - V_o = V_{in} - R_L i_L$$

$$\frac{di_L}{dt} = -\frac{R_L}{L} i_L + \frac{1}{L} V_{in}$$

$\underbrace{\phantom{-\frac{R_L}{L} i_L}}_B$

$$\text{For } 1-d(t): \quad \frac{di_L}{dt} = -\frac{R_L}{L} i_L + 0 V_{in}$$

$$\text{Average: } \frac{di_L}{dt} = -\frac{R_L}{L} i_L + \frac{1}{L} V_{in} d(t)$$

$$= -\frac{R_L}{L} i_L(t) + \frac{1}{L} (V_{in}(t) + d_D(t))$$

$$V_{in}(t) = V_{in} + v_{in}(t) \quad i_L(t) = I_L + i_s(t)$$

$$d_D(t) = D + d(t)$$

$$V_{in}(t) d_D(t) \approx V_{in} d(t) + D v_{in}(t) + DV_{in}$$

$$\frac{di_L}{dt} = 0 + \frac{di_L}{dt} = -\frac{R_L}{L} I_L - \frac{R_L}{L} i_s(t) + \frac{V_{in}}{L} d(t) + \frac{D}{L} v_{in} + DV_{in}$$

$$\text{Equate large signals. } -\frac{R_L}{L} I_L + \frac{DV_{in}}{L} = 0$$

$$V_o(t) = V_o + v_o(t) = R_L i_L(t)$$

$$V_o = R_L I_L = DV_{IN}$$

Operating
Q Point

Equate small signals:

$$\begin{aligned} \frac{d i_L}{dt} &= -\frac{R_L}{L} i_L + \frac{V_{IN}}{L} d(t) + \frac{D}{L} v_{in}(t) \\ &= -\frac{R_L}{L} i_L + \left[\frac{V_{IN}}{L} \quad \frac{D}{L} \right] \begin{bmatrix} d(t) \\ v_{in}(t) \end{bmatrix} \end{aligned}$$

$v_{in}(t)$ is a disturbance.

$d(t)$ is a control input. Use $d(t) = -K i_L(t)$

The pole is at $-\frac{R_L}{L} - \frac{V_{IN}}{L} K$.

See the trade off between speed and robustness.

Pick $K < 0$ to speed up the response, but watch out. What if R_L changes?

According to the Q point it won't change.

If the inductor has some winding resistance, it will have a voltage divider effect.

To compensate D will be larger.

Without C in the output there should be no discontinuous conduction mode.

